 




Unit-3: 8085 Microprocessor



© 2019 Darshan Institute of Engineering & Technology. All rights reserved.



Prof. Swati R Sharma

Computer Engineering Department

Darshan Institute of Engineering & Technology, Rajkot

✉ swati.sharma@darshan.ac.in

☎ (0) 9727747317



Subject Overview

Sr. No.	Unit	% Weightage
1	Introduction to Microprocessor	8%
2	Microprocessor Architecture and Operations	7%
3	8085 Microprocessor	12%
4	Assembly Language Programming Basics	13%
5	8085 Assembly Language Programs	12%
6	Stack & Subroutines	13%
7	I/O Interfacing	20%
8	Advanced Microprocessors	15%



Topics to be covered

- Introduction to 8085
- 8085 Programming Model
- Bus Organization of 8085
- 8085 pin diagram
- 8085 Architecture/Block Diagram
- T-States, Machine and Instruction Cycle
- Demultiplexing Address and Data Bus AD0-AD7
- Timing Diagram
- Memory Interfacing
- Generating Control Signals



Introduction to 8085

Introduction to 8085

- 8085 is pronounced as "eighty-eighty-five" microprocessor.
- It is an 8-bit microprocessor designed by Intel in 1977 using NMOS technology.

Introduction to 8085


- 8 bit General purpose microprocessor (i.e. 8 bit data bus).
- It is a single chip N MOS device with 40 pins.
- It has multiplexed address and data bus.($AD_0 - AD_7$).
- It works on 5-Volt DC power supply.
- The maximum clock frequency is 3MHz while minimum frequency is 500kHz.
- It provides 16 address lines, therefore capable of addressing $2^{16} = 64K$ of memory.
- It supports external interrupt request.
- It has two 16 bit registers named program counters (PC) and stack pointer (SP).

Introduction to 8085

- It generates 8 bit I/O address so it can access $2^8 = 256$ input ports.
- It provides 5 hardware interrupts:
 1. TRAP
 2. RST 5.5
 3. RST 6.5
 4. RST 7.5
 5. INTR
- It provides accumulator, 5 flag register, 6 general purpose registers and 2 special purpose registers (SP, PC).

8085 Programming Model

8085 Programming Model

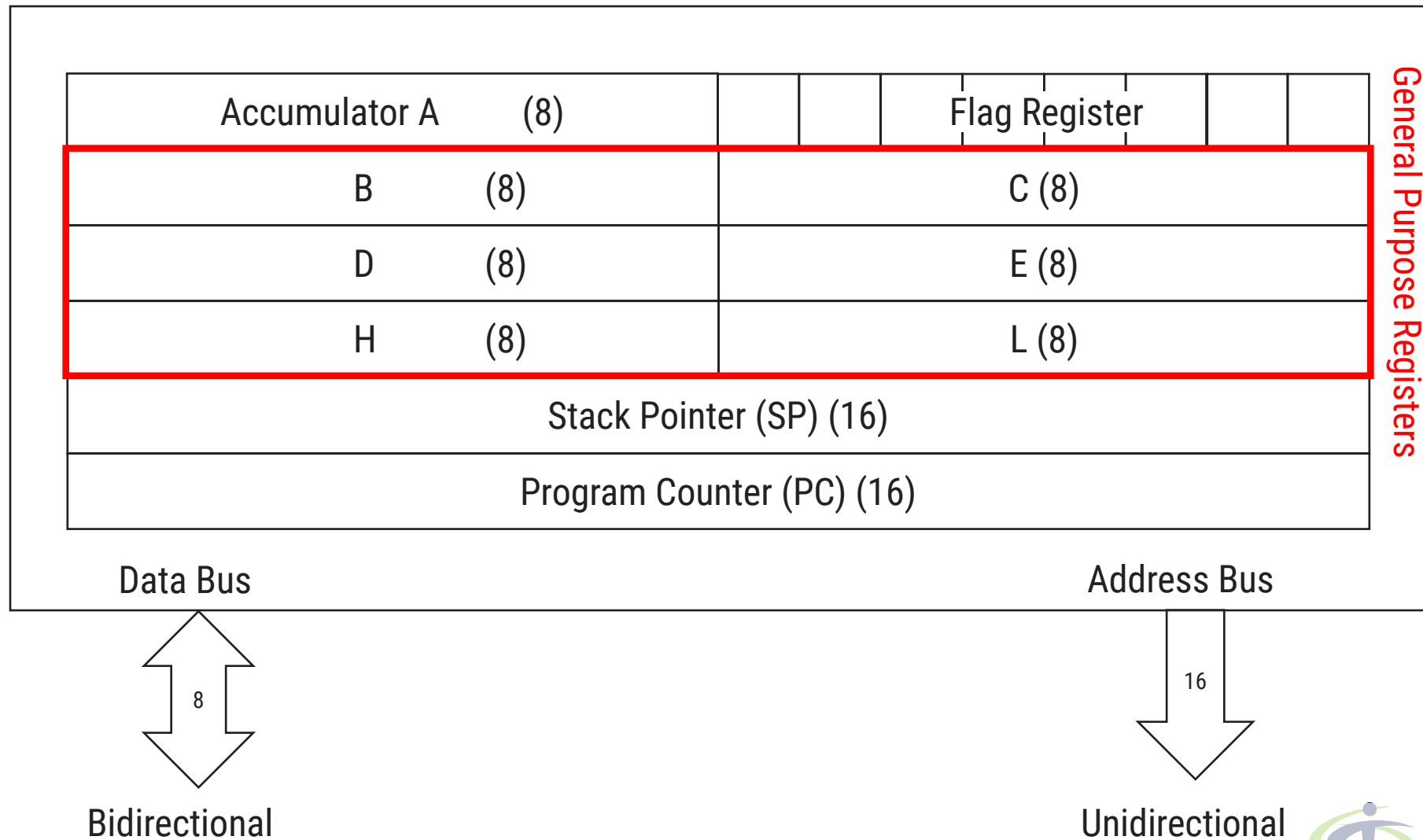


General Purpose Registers

- 6 general purpose registers to store 8-bit data **B, C, D, E, H & L**.
- Can be combined as fixed register pairs – **BC, DE, HL** to perform **16** bit operations.
- Used to store or copy data using data copy instructions.


B (8)	C (8)
D (8)	E (8)
H (8)	L (8)

8085 Programming Model

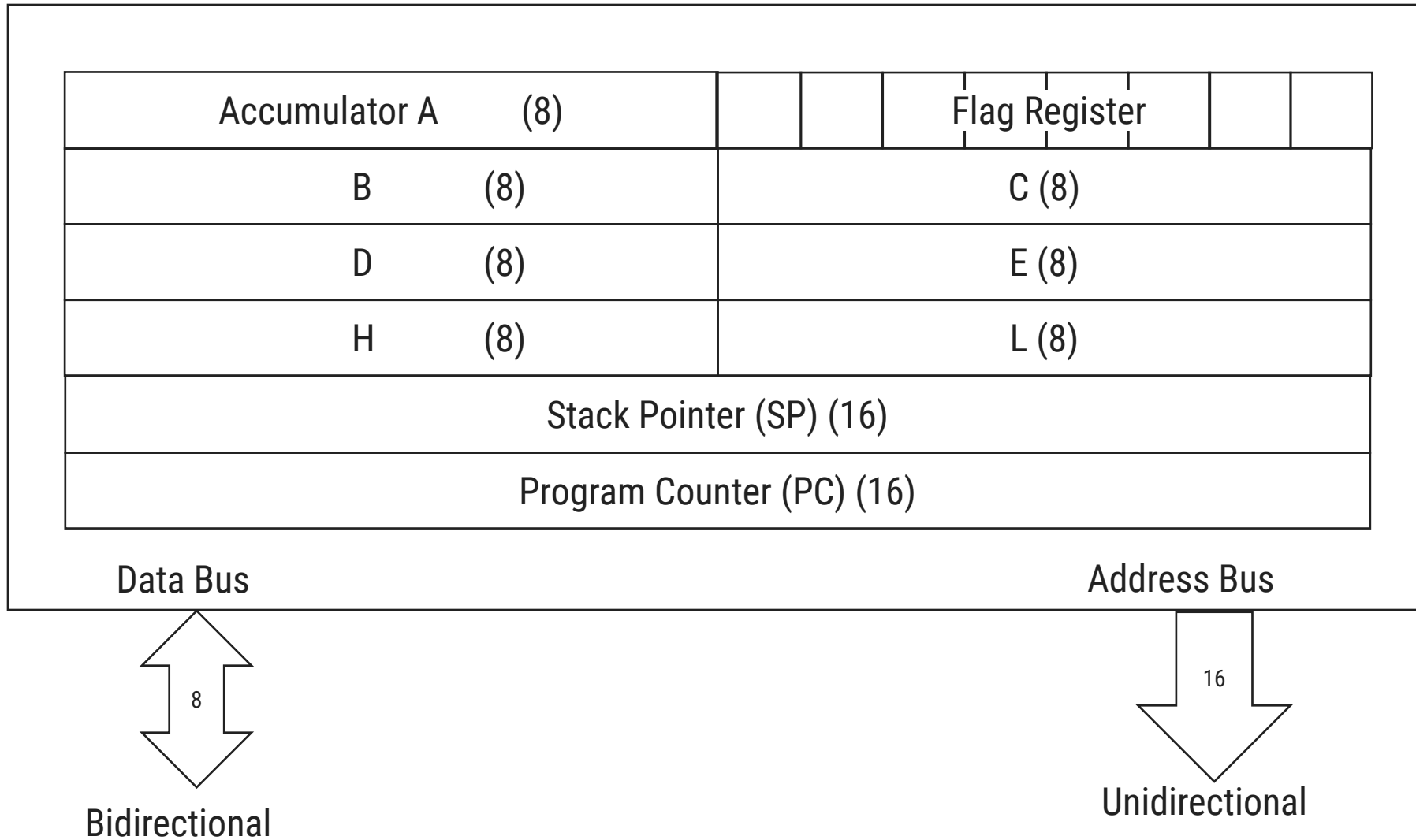


Accumulator

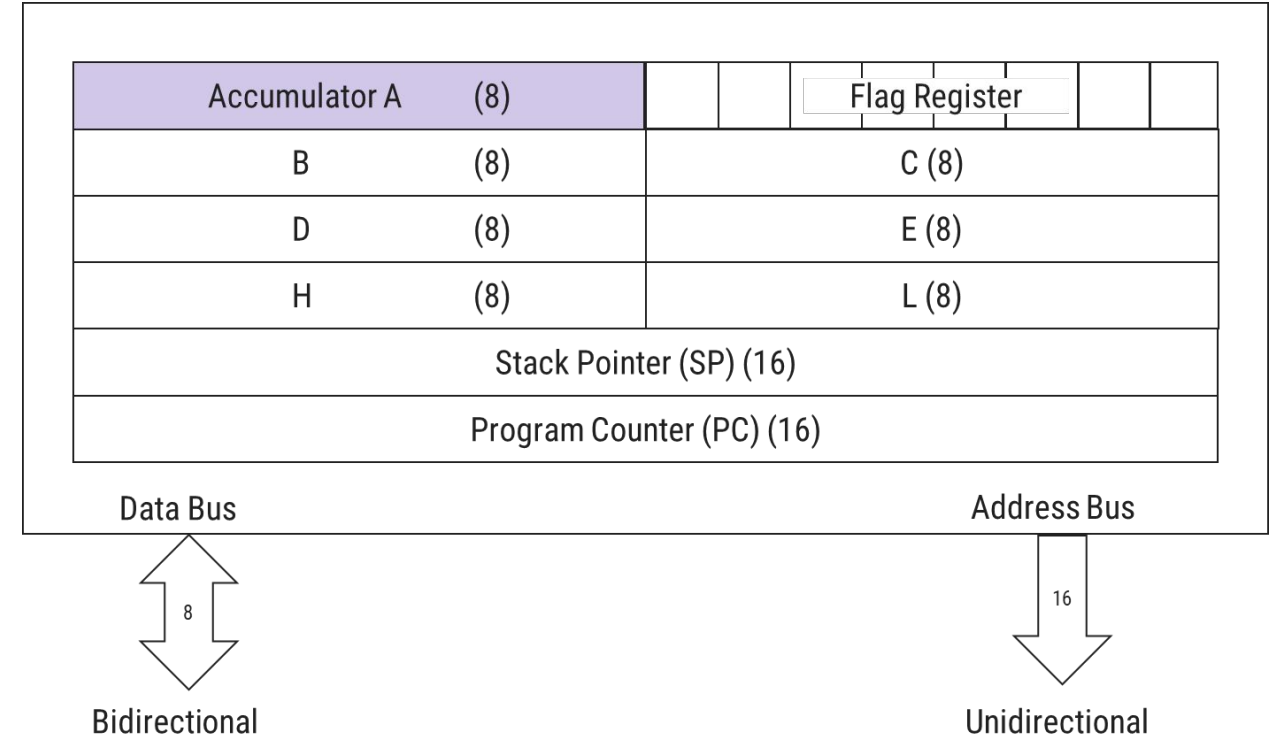- 8 - bit register, identified as **A**
- Part of ALU
- Used to store 8-bit data to perform **arithmetic & logical** operations.
- Result of operation is stored in **Accumulator**.



8085 Programming Model

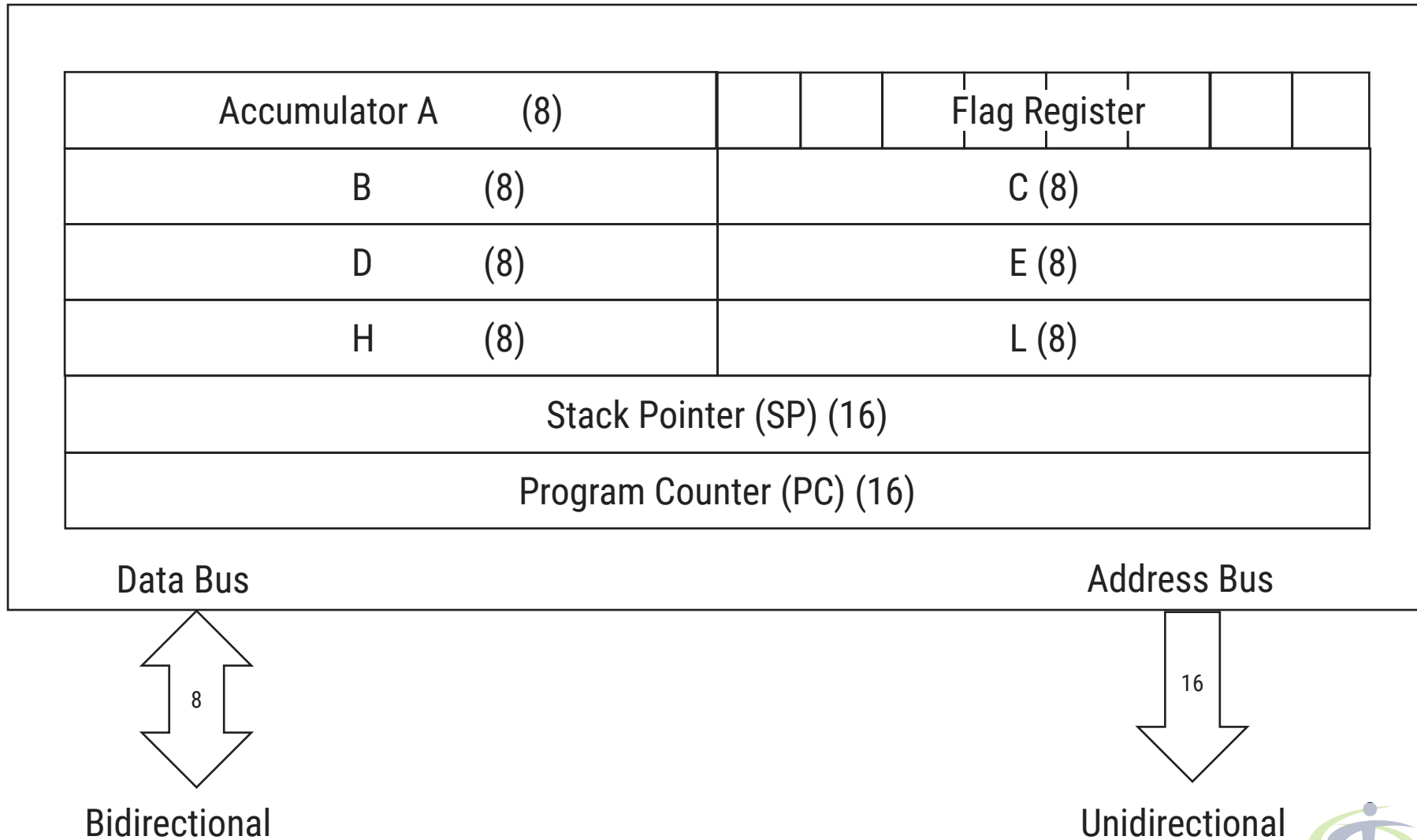

Flag Register

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
S	Z	X	AC	X	P	X	CY

X:Undefined

S -Sign Flag

Set (1) if 7th bit of result is 1;
otherwise reset (0)

1 0 1 0 1 0 1 0
S = 1

Z -Zero Flag

Set (1) when result is zero;
otherwise reset(0)

1 0 1 0
- 1 0 1 0

0 0 0 0
Z = 1

P -Parity Flag

Set (1) if result has even no. of 1's &
Reset(0) if result has odd no. of 1's

1 0 0 1 0 0 1 1
P = 1
AC -Auxiliary Carry Flag
Set (1) when carry bit is
generated by 3rd bit &
passed to bit 4th bit.

1 1 1
0 0 1 0 1 0 1 0
+ 0 1 1 0 1 0 0 1

1 0 0 1 0 0 1 1
AC = 1

CY -Carry Flag

Set (1) if arithmetic
operation results in
carry;
otherwise reset(0)

1 1 1
1 0 1 0 1 0 1 0
+ 0 1 1 0 1 0 0 1


1 0 0 0 1 0 0 1
CY = 1

Flag Register


- ALU has 5 Flag Register that set/reset after an operation according to data conditions of the result in accumulator & other registers.
- Helpful in decision making process of microprocessor.
- Conditions are tested through software instructions.

For e.g.

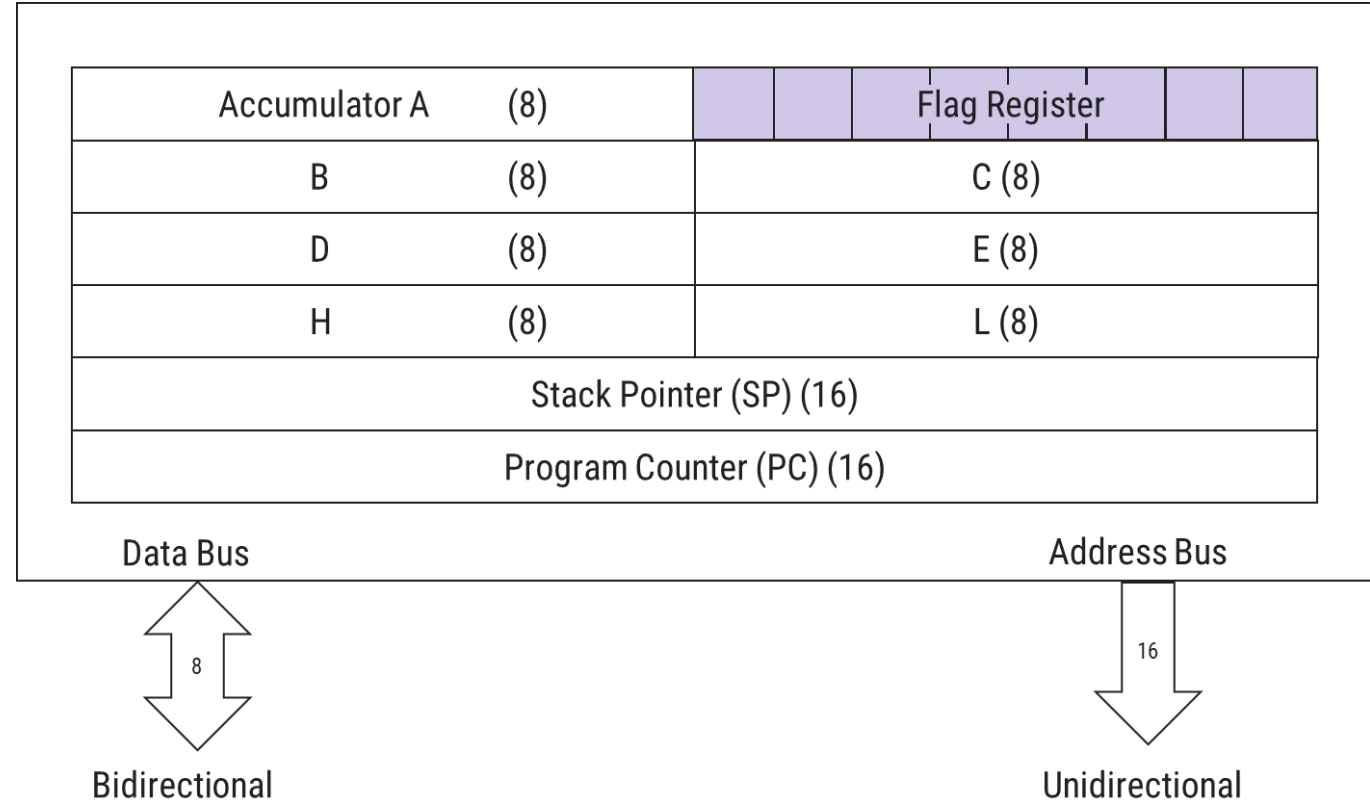JC (Jump On Carry) is implemented to change the sequence of program when **CY**(Carry Flag) is set(1).



8085 Programming Model

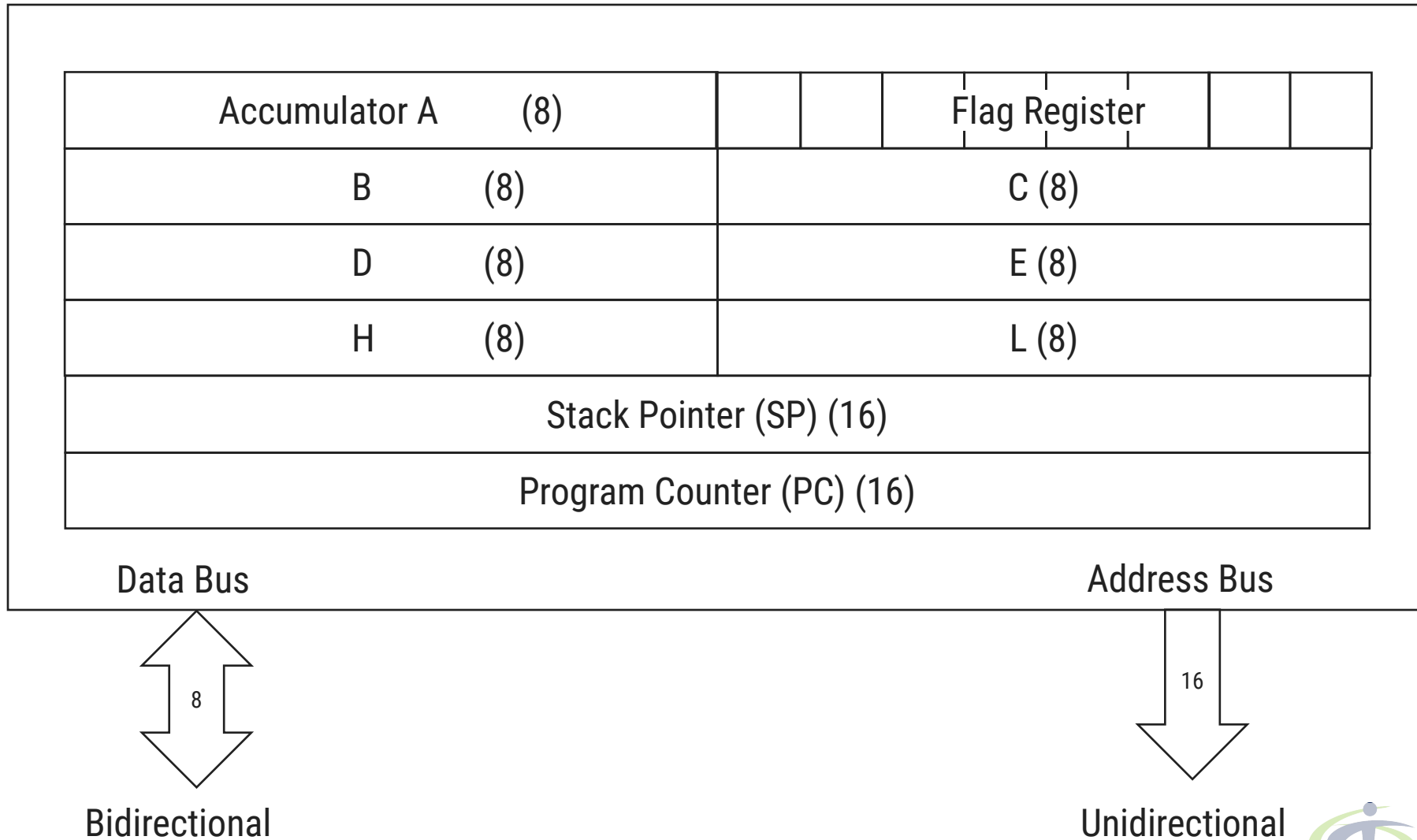


Stack Pointer & Program Counter

Stack Pointer(SP)

- Used as **memory pointer**.
- Points to the memory location in R/W memory, called **Stack**.
- Beginning of stack is defined by loading a 16-bit address in the stack pointer.

Program Counter(PC)

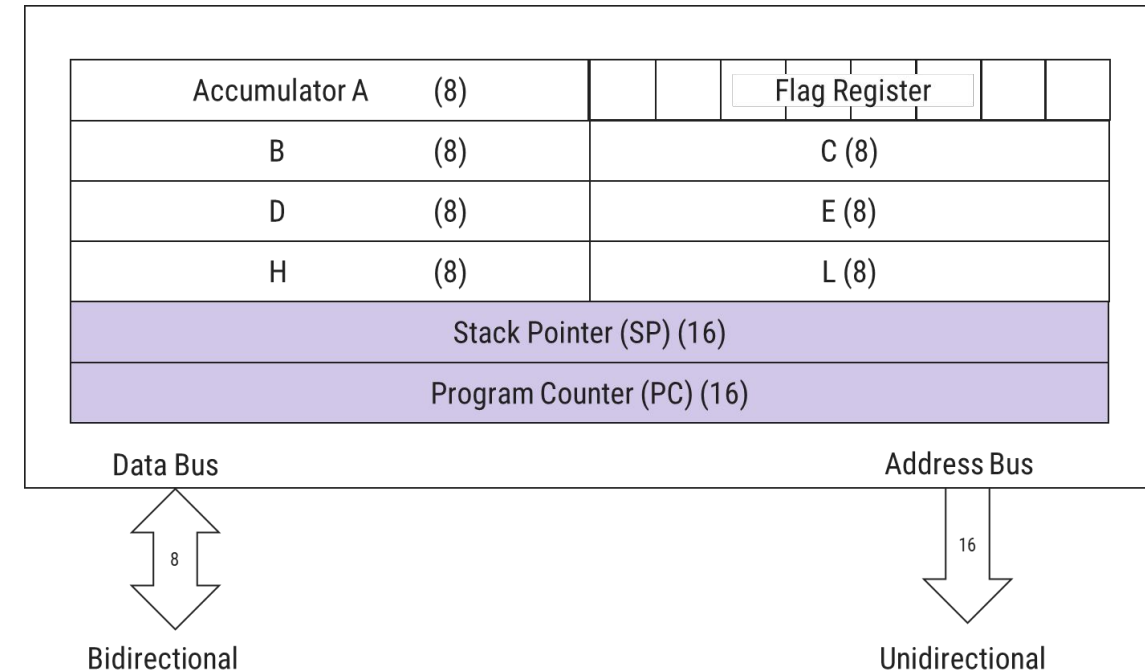
- Microprocessor uses PC register to **sequence** the execution of instructions.
- Its function is to point to memory address from which **next byte is to be fetched**.
- When a byte is being fetched, PC is **incremented** by **1** to point next memory location.




GTU Que: Explain 8085 Programming Model and flag register.[7m] (W'18,W'19)

Bus Organization of 8085

System bus

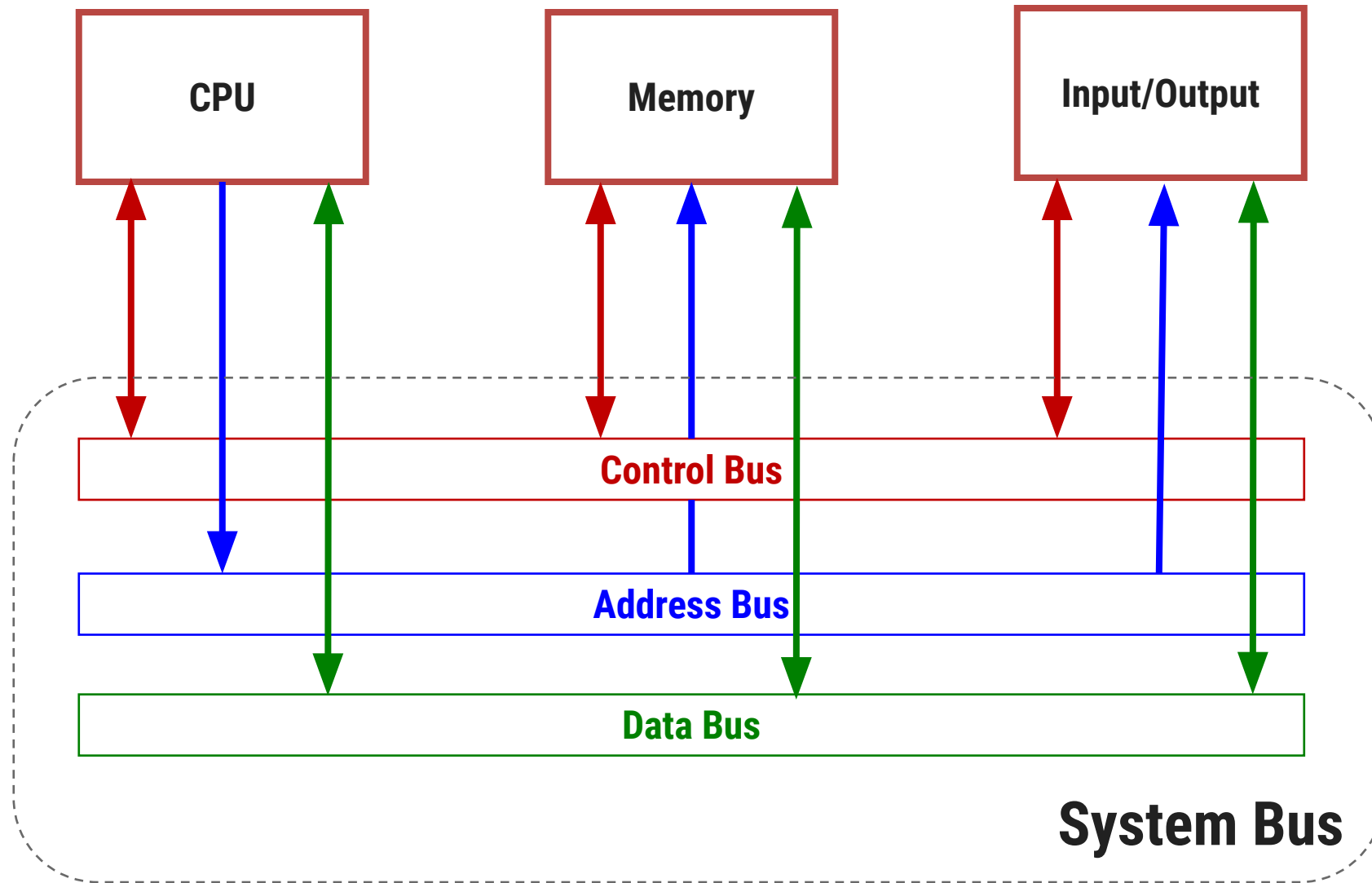


Bus Organization of 8085

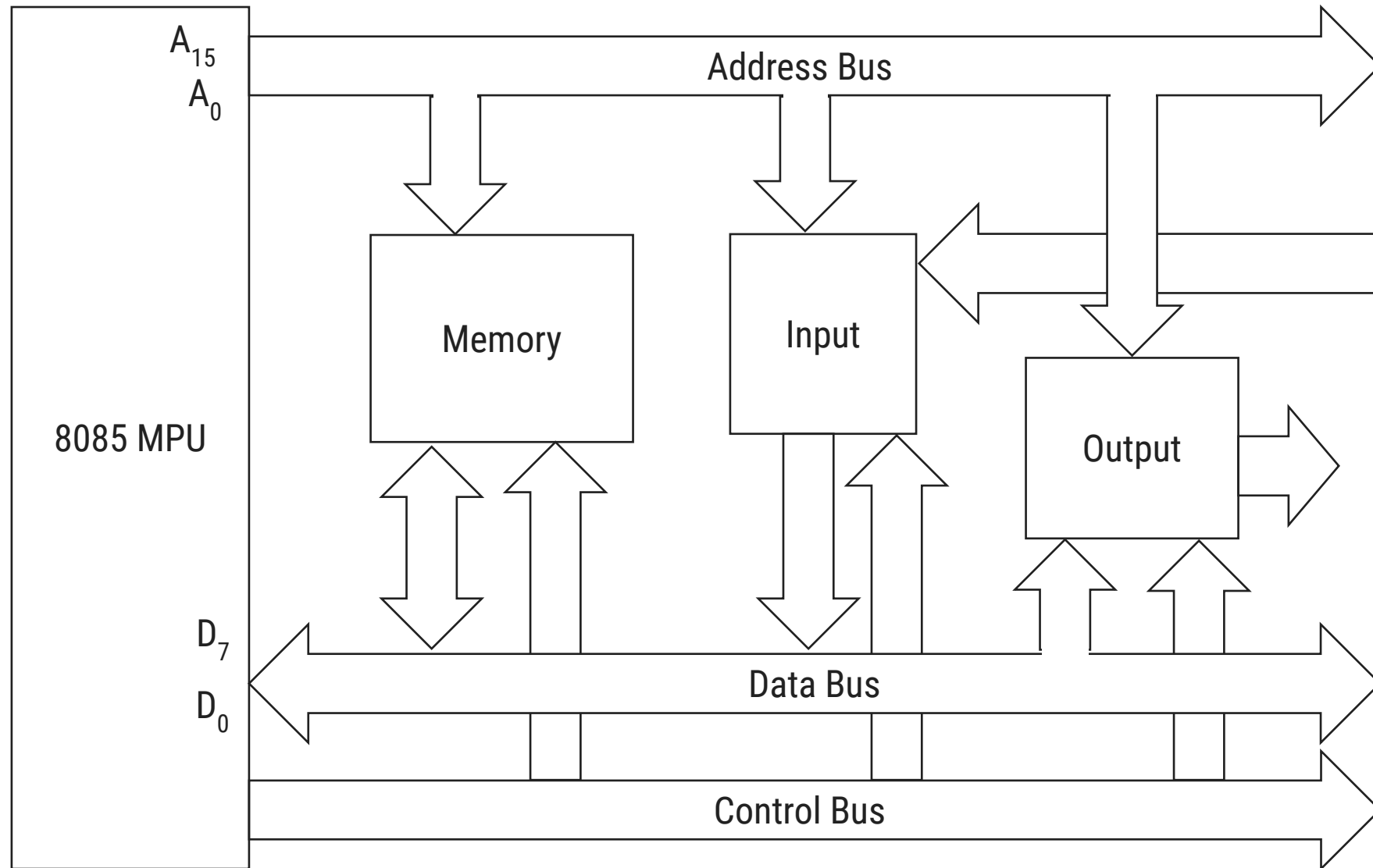


Address bus

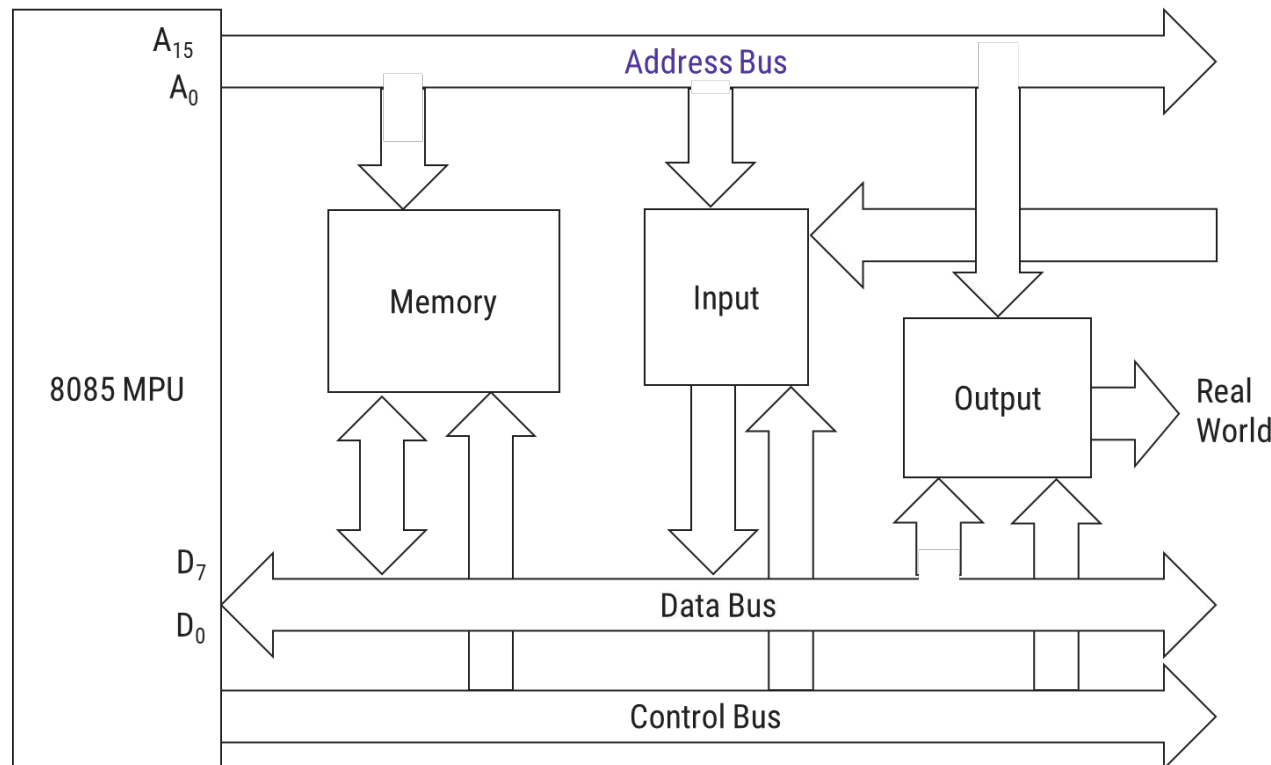- Group of 16 **unidirectional** lines generally identified as A_0 to A_{15} .
i.e. bits flow from microprocessor to peripheral devices.
- 16 address lines are capable of addressing **65536** memory locations. So, 8085 has **64K** memory locations.




HEX	FFFF
DEC	65,535
OCT	177 777
BIN	1111 1111 1111 1111

Bus Organization of 8085

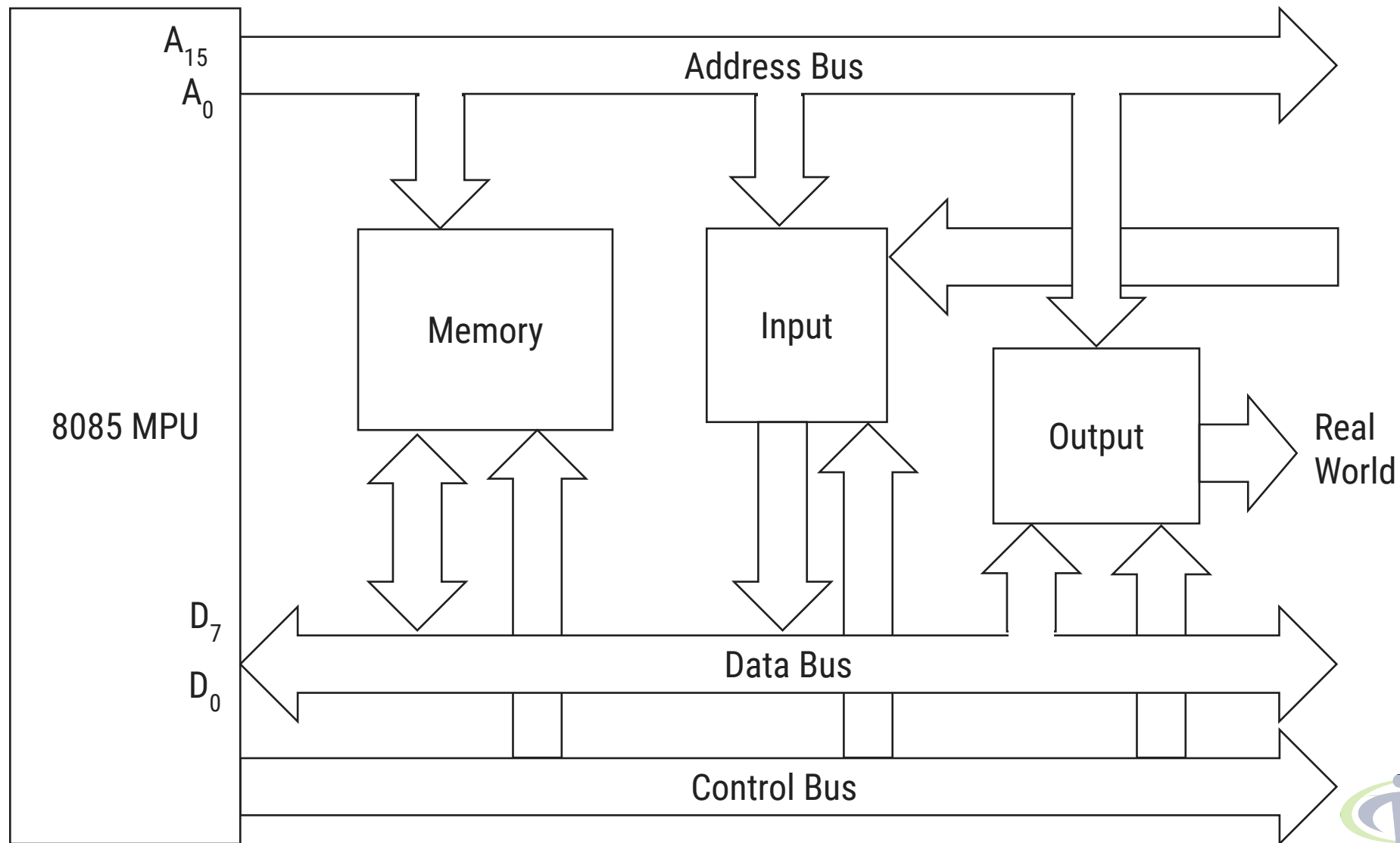


Data bus

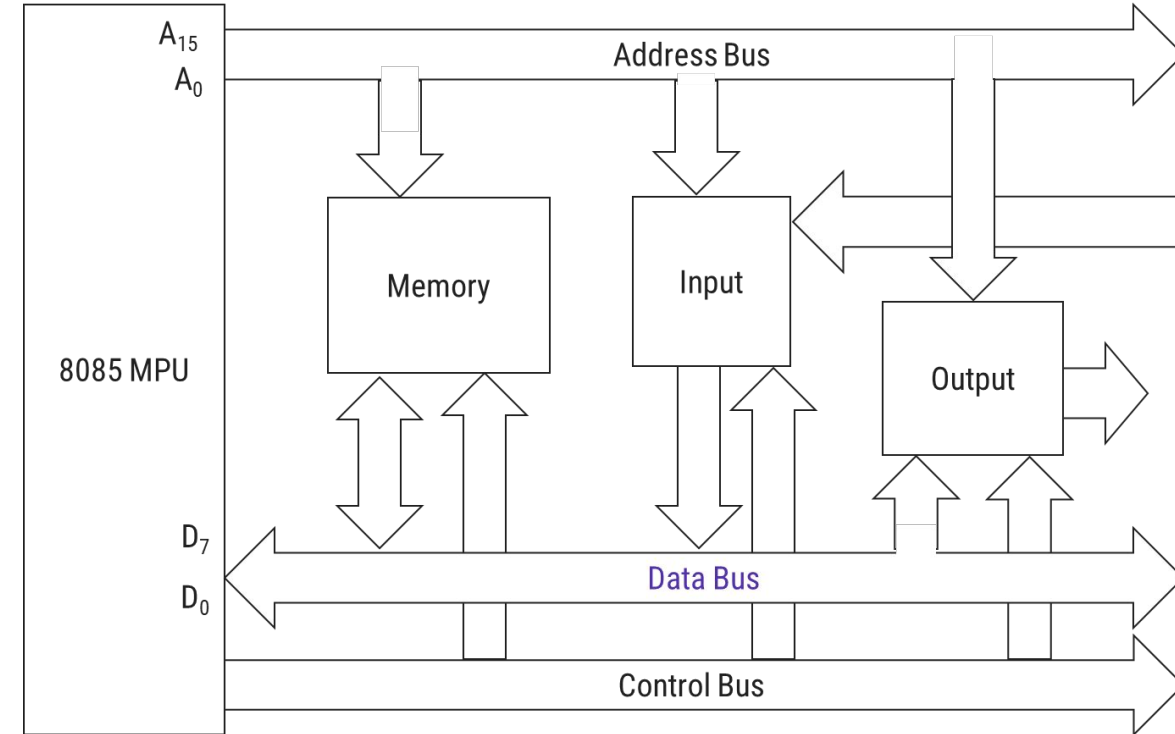- Group of 8 lines identified as D_0 to D_7 .
- They are bidirectional i.e. data flow in both directions between microprocessor, memory & peripheral.
- 8 data lines enable microprocessor to manipulate data ranging from 00 H to FF H ($2^8=256$ numbers).
- Largest number appear on data bus is $1111\ 1111 \Rightarrow (255)_{10}$.
- As Data bus is of 8-bit, 8085 is known as 8-bit Microprocessor.





Bus Organization of 8085

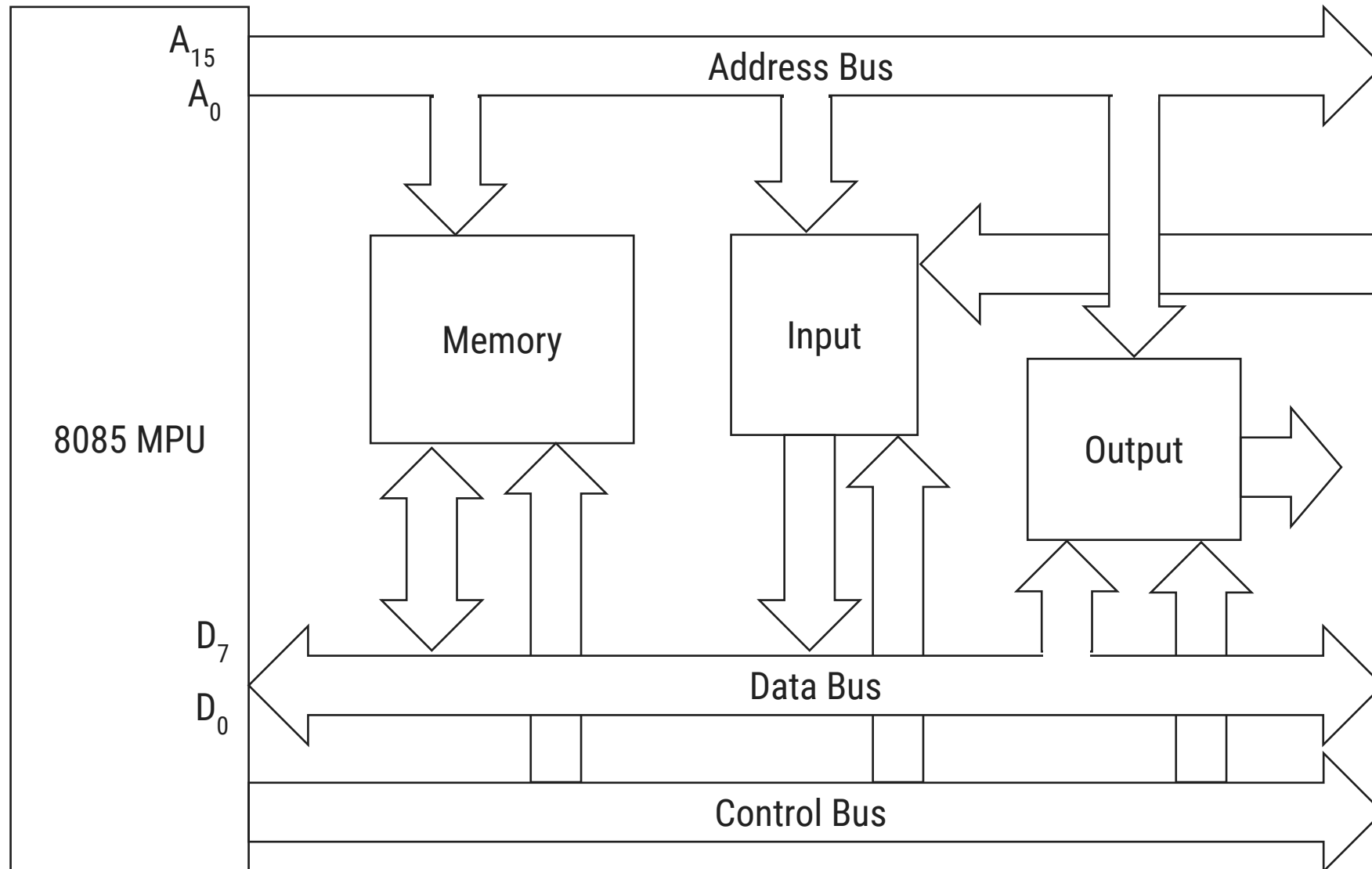

Control bus

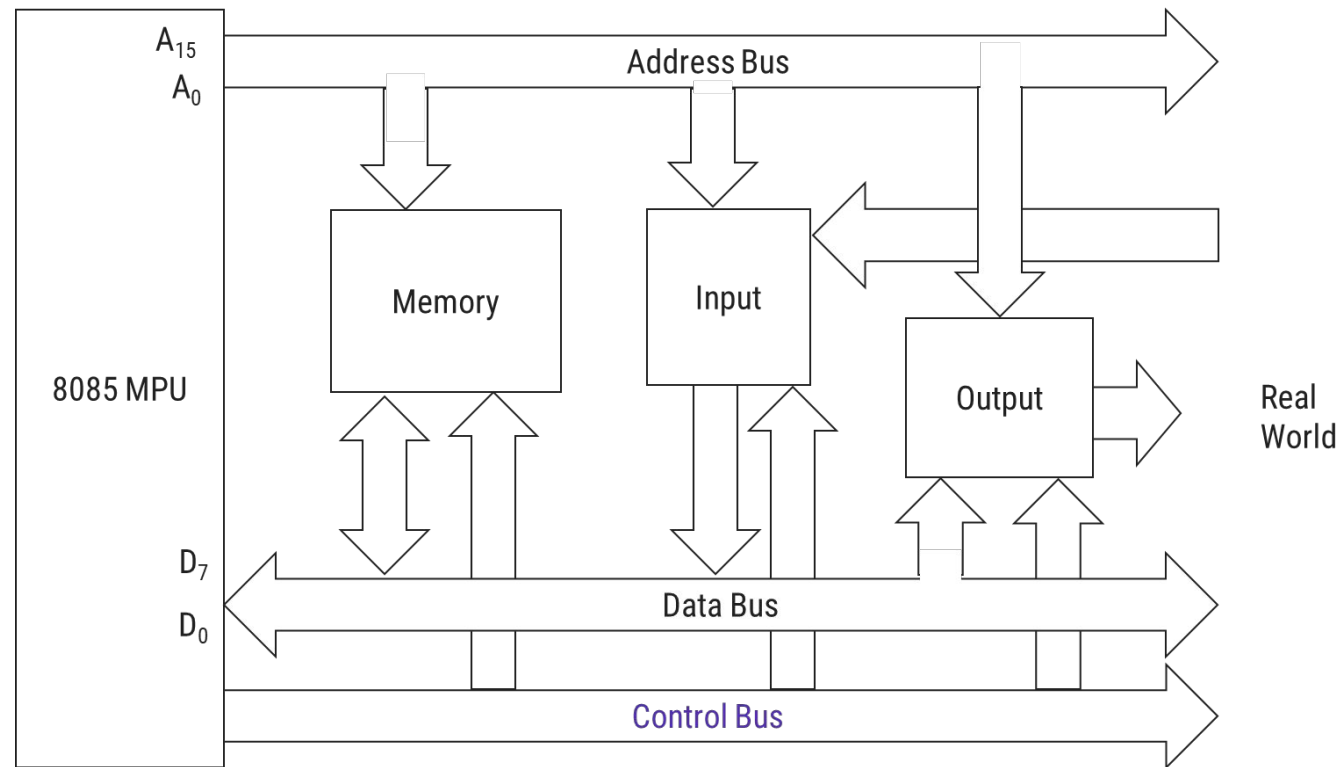
- It comprises of various single lines that carry **synchronization, timing & control signals**.
- These signals are used to identify a device type with which MPU intends to communicate.
- Some control signals are **Read, Write** and **Opcode fetch** etc.



 

8085 pin diagram

8085 pin diagram

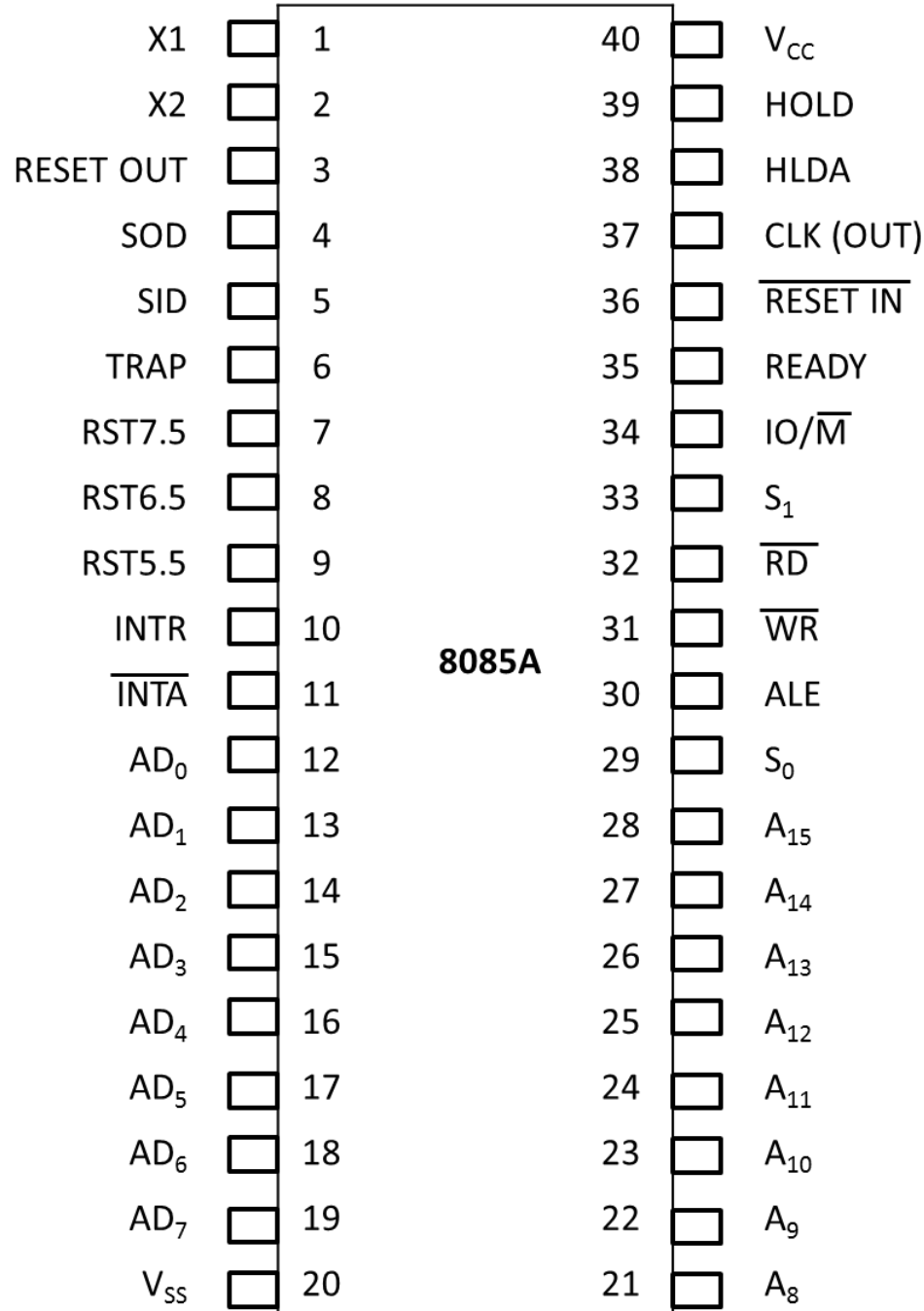


- 8-bit general purpose microprocessor.
- Capable of addressing 64K of memory.
- It has 40 pins.
- Requires +5V single power supply.

8085 pin diagram


Signals are classified into 6 groups:

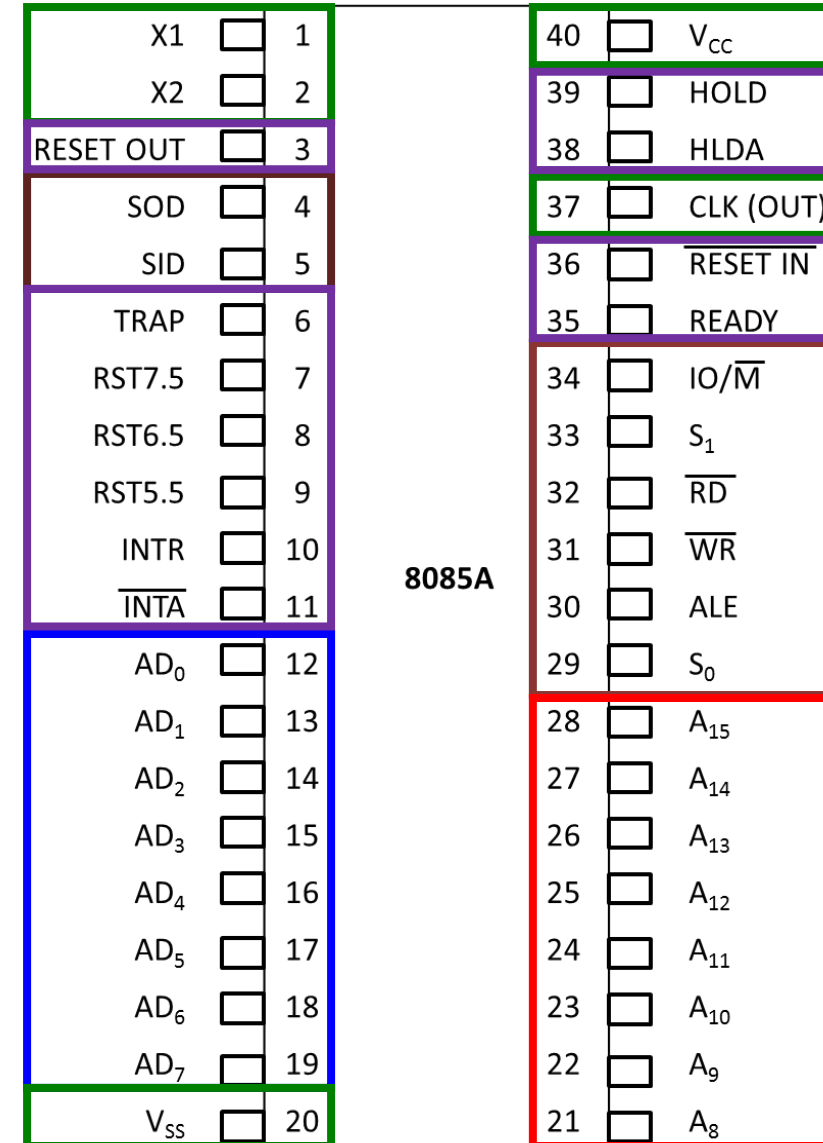1. Address bus
2. Multiplexed address/data bus
3. Control & status signals
4. Power supply & frequency signals
5. Externally initiated signals
6. Serial I/O ports




8085 pin diagram: Address Bus

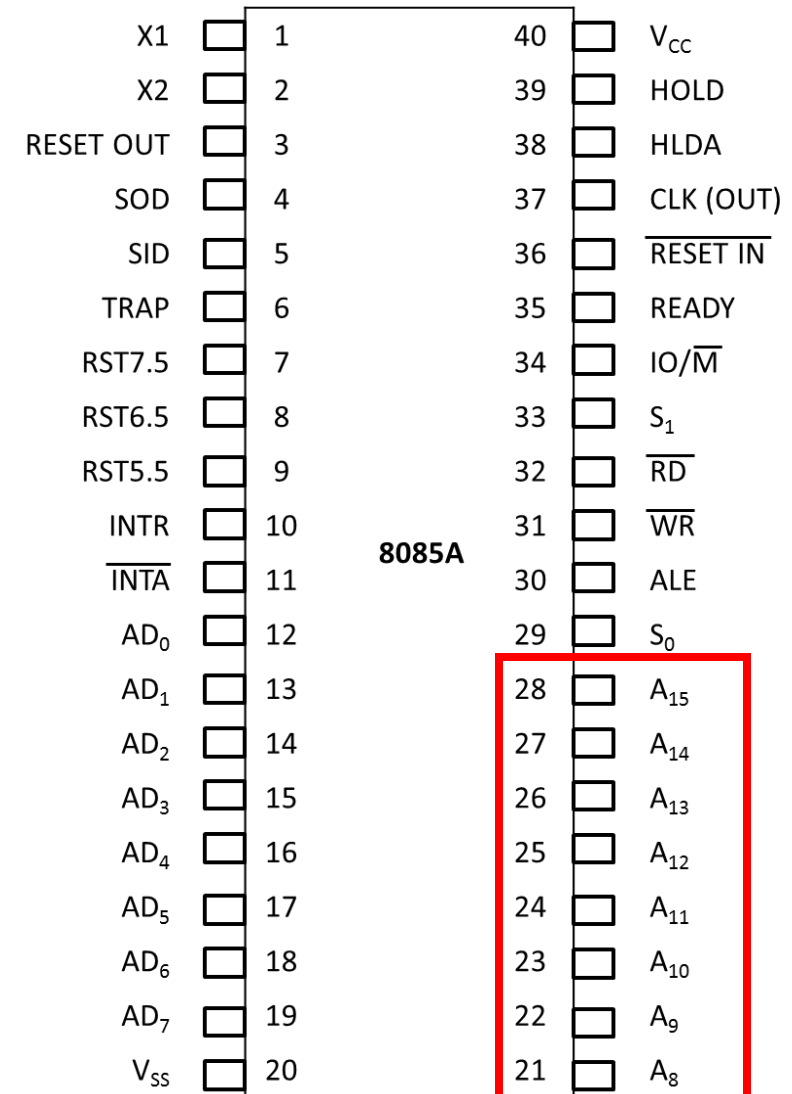- 16 signal lines are used as address bus.
- However these lines are split into two segments:
 $A_{15} - A_8$ and $AD_7 - AD_0$
- $A_{15} - A_8$ are unidirectional and used to carry high-order address of 16-bit address.
- $AD_7 - AD_0$ are used for dual purpose.



8085 pin diagram: Multiplexed Address/Data Bus

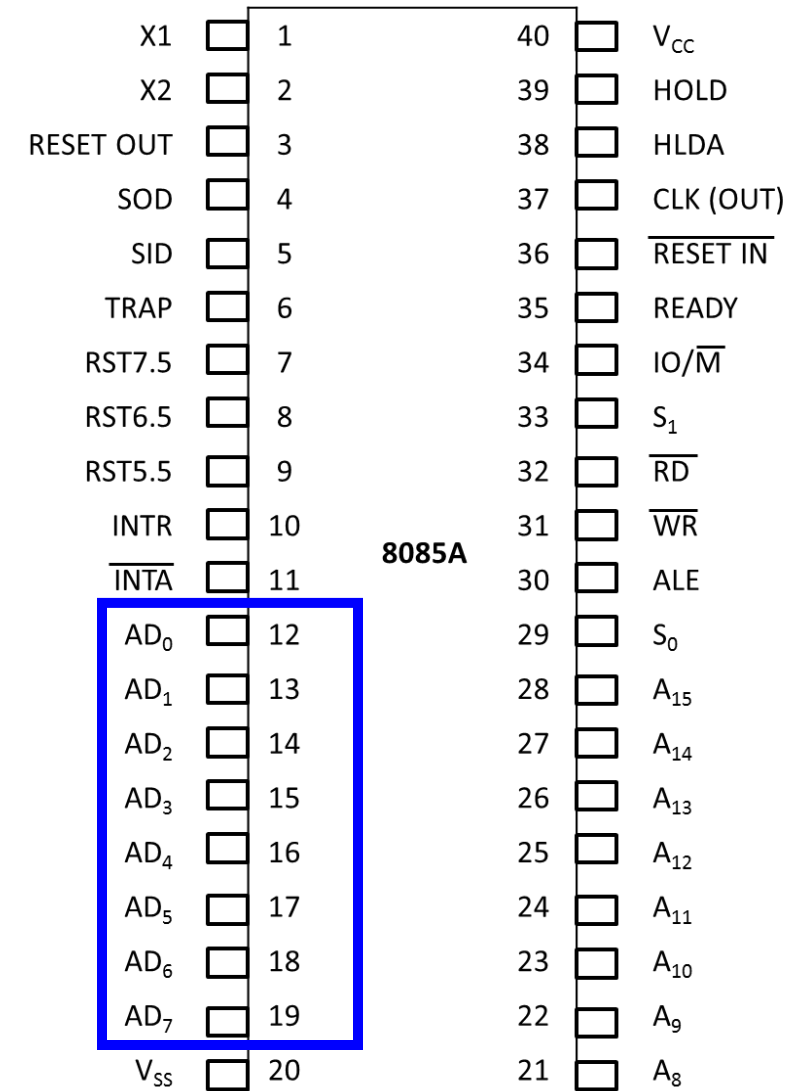- Signal lines AD_7 - AD_0 are bidirectional and serve dual purpose.
- They are used as **low-order address bus** as well as **data bus**.
- The low-order address bus can be separate from these signals by using a latch (**ALE**).



8085 pin diagram: Control & Status Signals

To identify nature of operation

□ Two Control Signals


1. \overline{RD} (Read)
2. \overline{WR} (Write)

□ Three Status Signals

1. S_1
2. S_0
3. IO/\overline{M}

□ To indicate beginning of operation

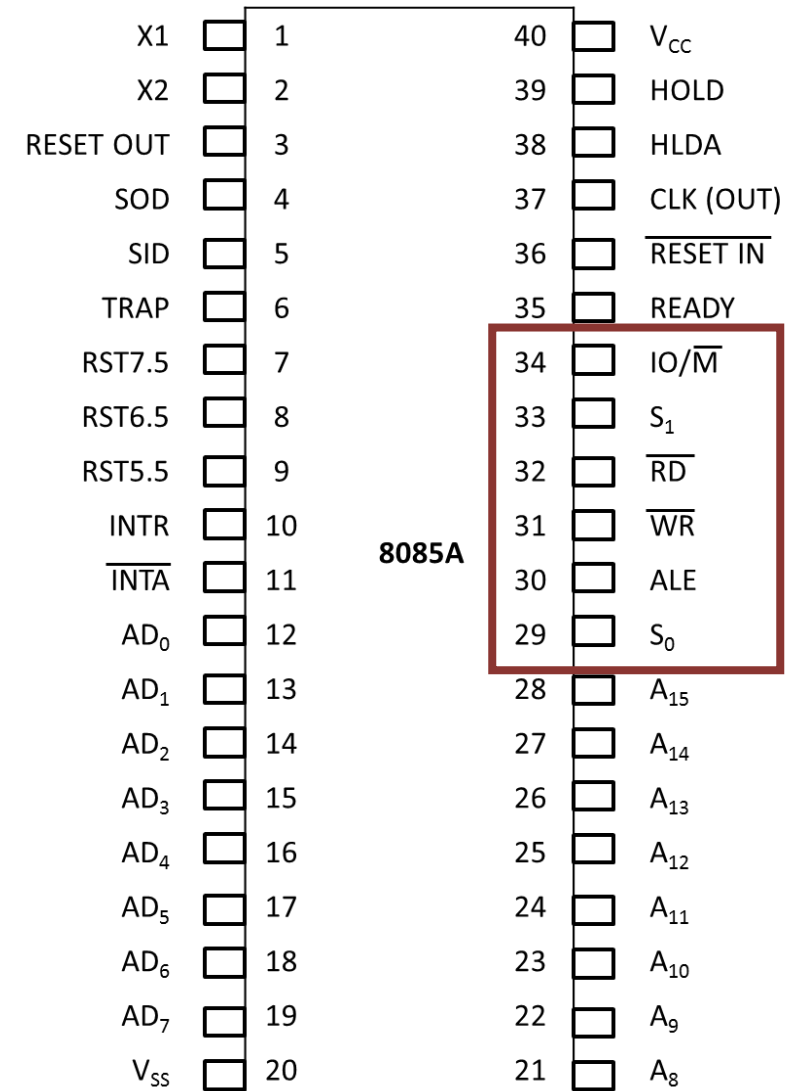
1. ALE(Address Latch Enable)
ALE \leftarrow 1, then Address bus
ALE \leftarrow 0, then Data bus



8085 pin diagram: Control & Status Signals

ALE: Pin 30

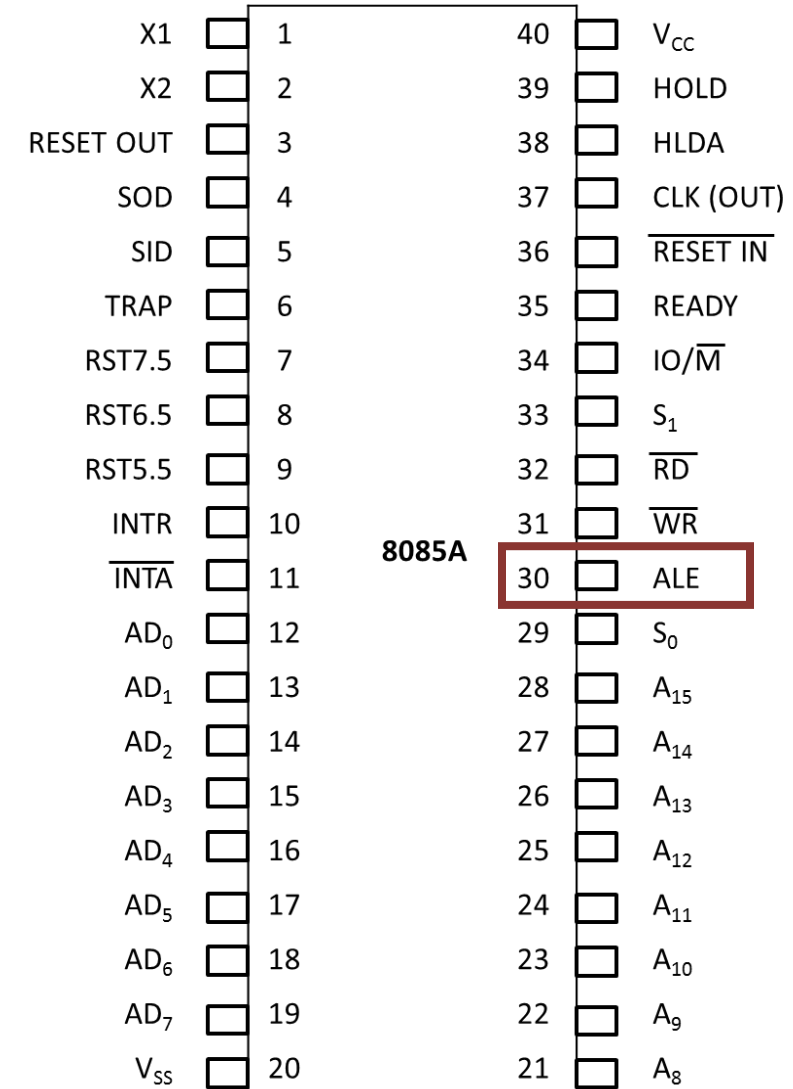
- This is positive going pulse generated every time the 8085 begins an operation (machine cycle).
- It indicates that the bits on AD_7-AD_0 are address bits.
- This signal is used primarily to latch the low-address from multiplexed bus & generate a separate set of address lines A_7-A_0 .



8085 pin diagram: Control & Status Signals

\overline{RD} (Read): Pin 32

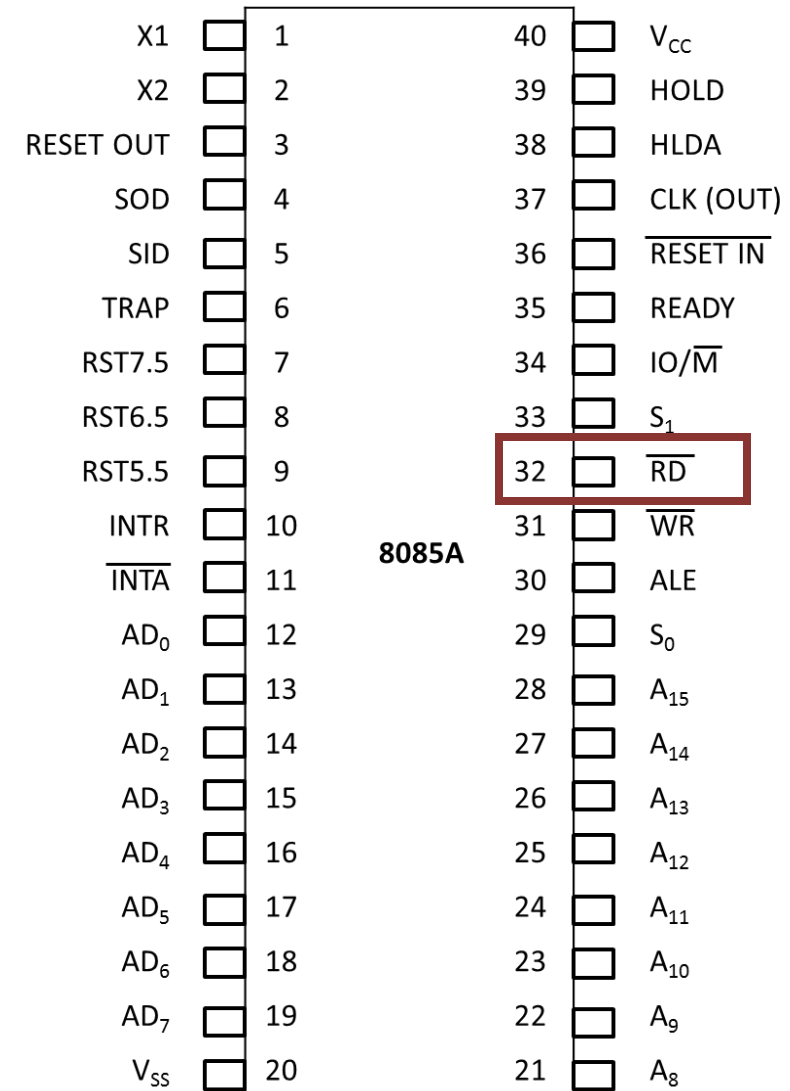
- This is a read control signal (active low)
- This signal indicates that the selected I/O or Memory device is to be **read** & data is available on data bus.



8085 pin diagram: Control & Status Signals

WR (Write): Pin 31

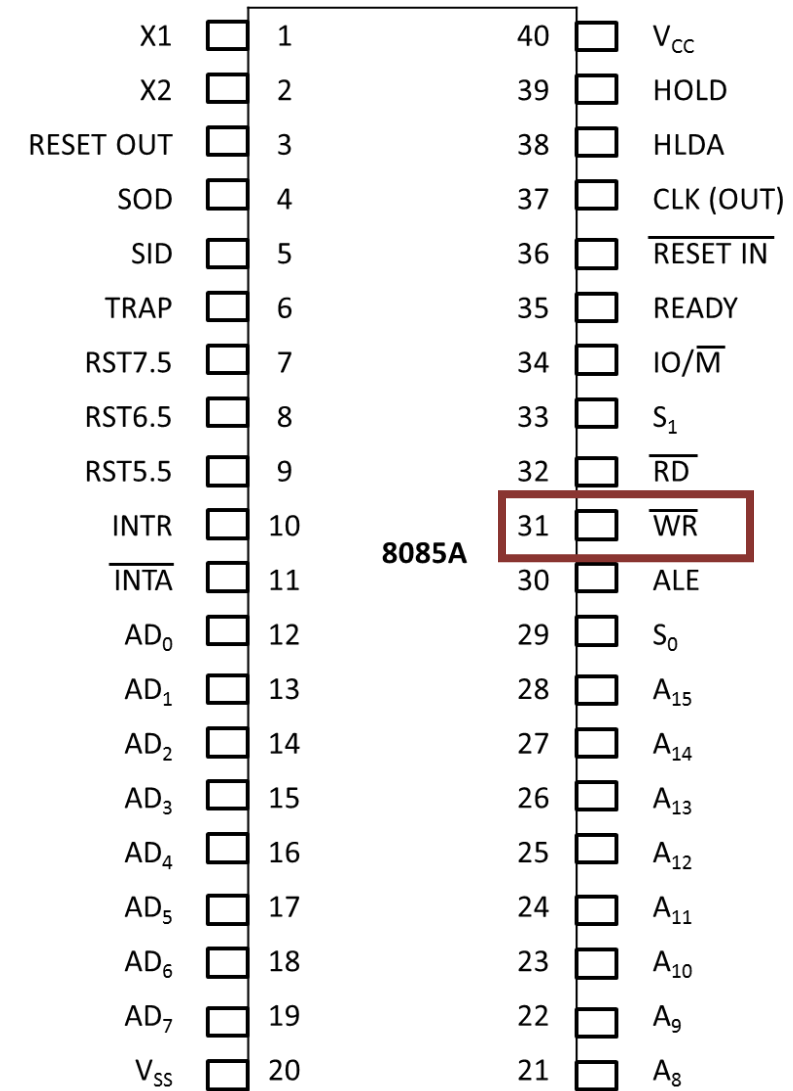
- This is a write control signal (active low)
- This signal indicates that the selected I/O or Memory device is to be **write** & data is available on data bus.



8085 pin diagram: Control & Status Signals

$\overline{\text{IO/M}}$: Pin 34

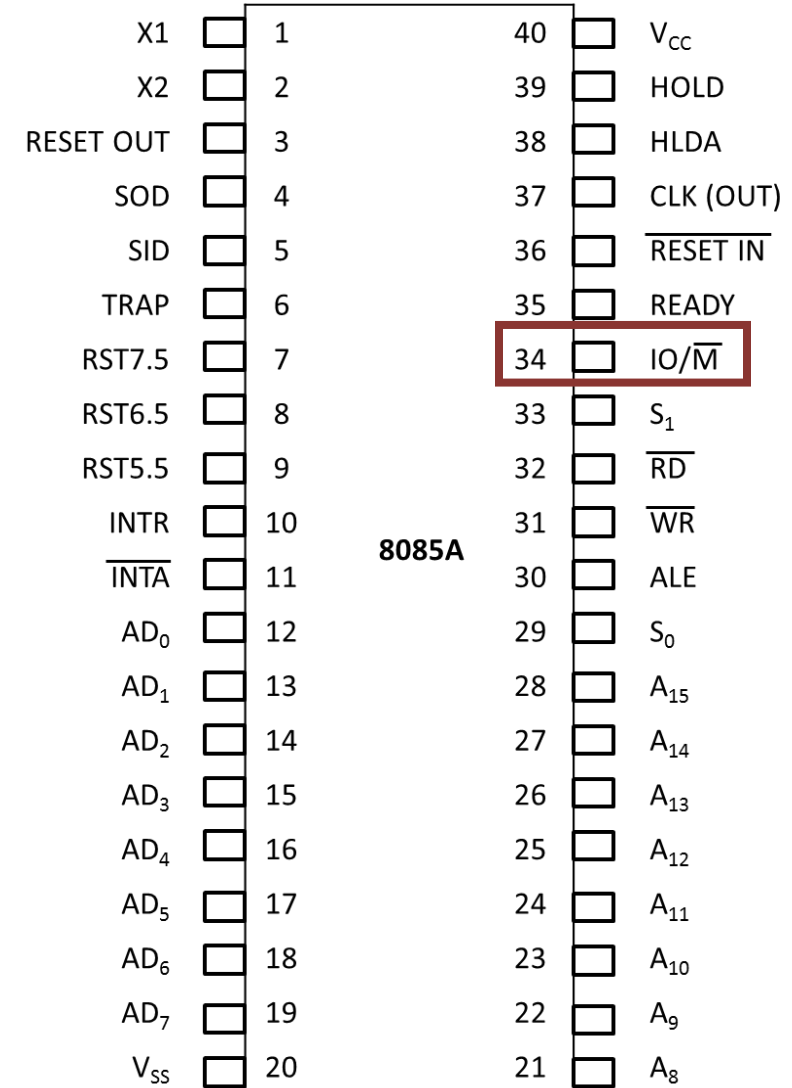- This is a status signal used to differentiate I/O and memory operation.
- When signal is
 - high \rightarrow I/O operation
 - low \rightarrow Memory operation
- This signal is combined with $\overline{\text{RD}}$ and $\overline{\text{WR}}$ to generate I/O & memory control signals.




8085 pin diagram: Control & Status Signals

S_1 (Pin 33) & S_0 (Pin 29)

□ These status signals can identify various operations.

S_1	S_0	Mode
0	0	HLT
0	1	WRITE
1	0	READ
1	1	OPCODE FETCH

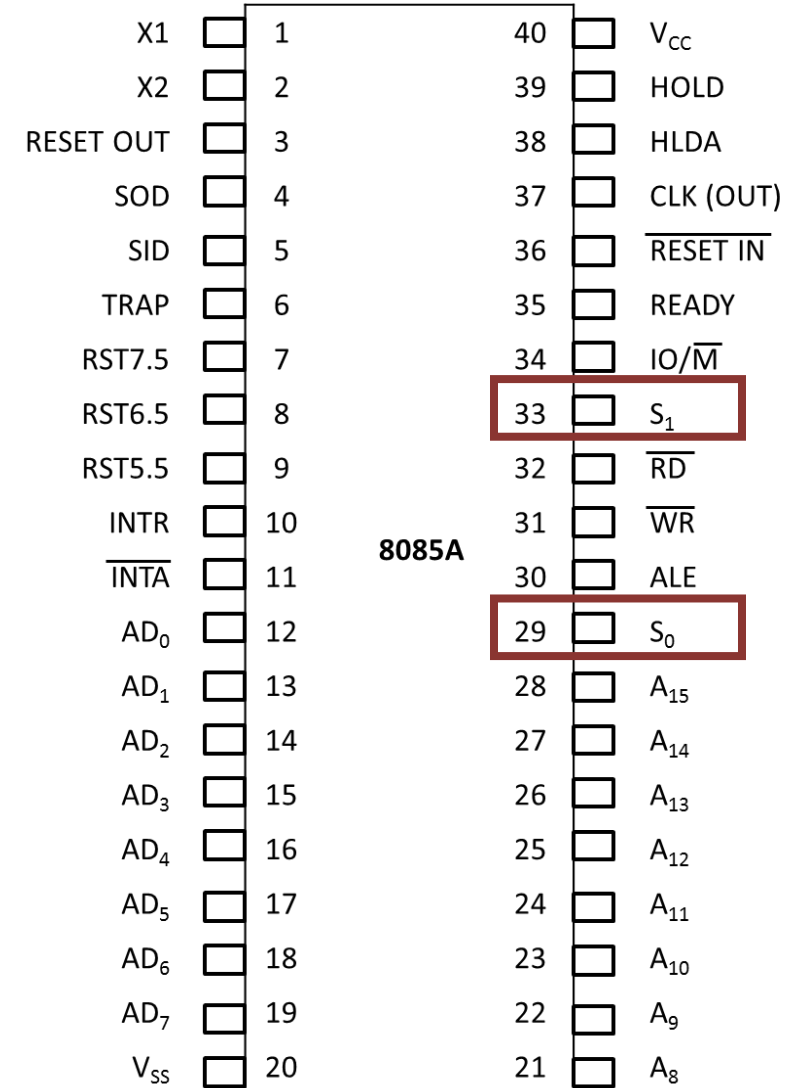


8085 pin diagram

$\overline{IO/\overline{M}}$	\overline{RD}	\overline{WR}	Operation
0	0	0	HLT
0	0	1	\overline{MEMR}
0	1	0	\overline{MEMW}
0	1	1	Opcode Fetch
1	0	0	HLT
1	0	1	\overline{IOR}
1	1	0	\overline{IOW}
1	1	1	NOP

8085 Pin Diagram: Power Supply & Frequency Signal


□ V_{cc} → Pin 40, +5V Supply.

□ V_{ss} → Pin 20, Ground Reference

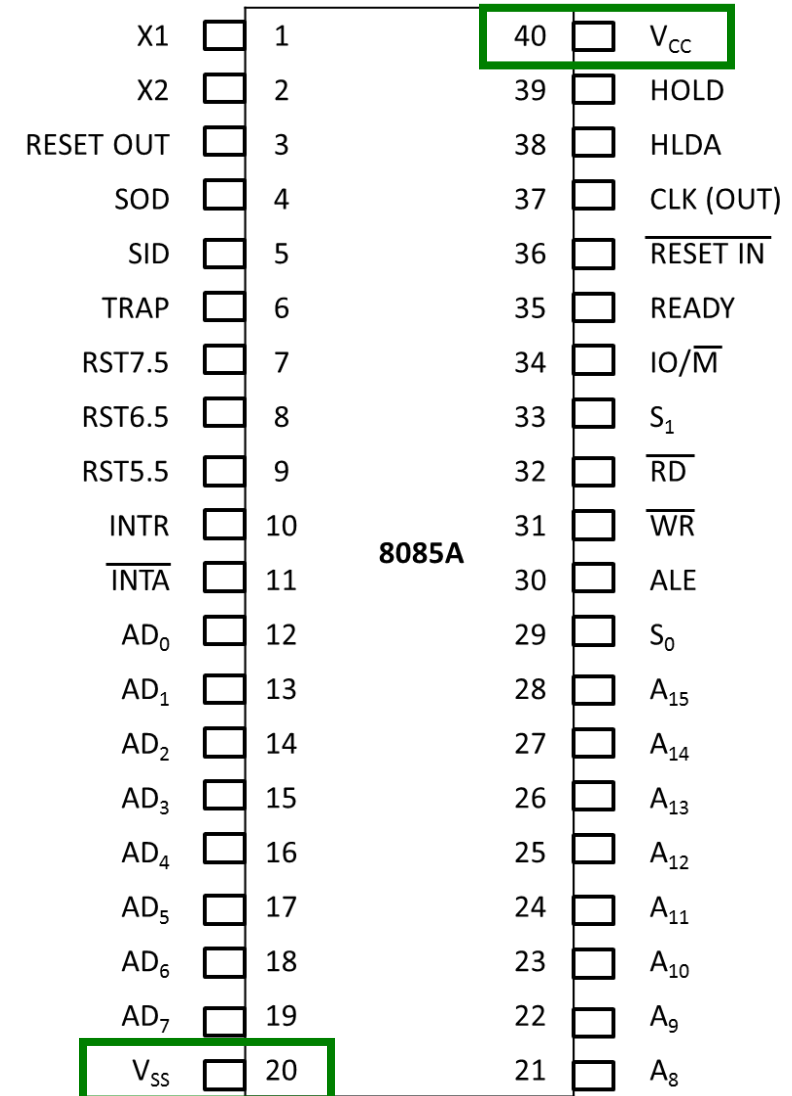

8085 Pin Diagram: Power Supply & Frequency Signal


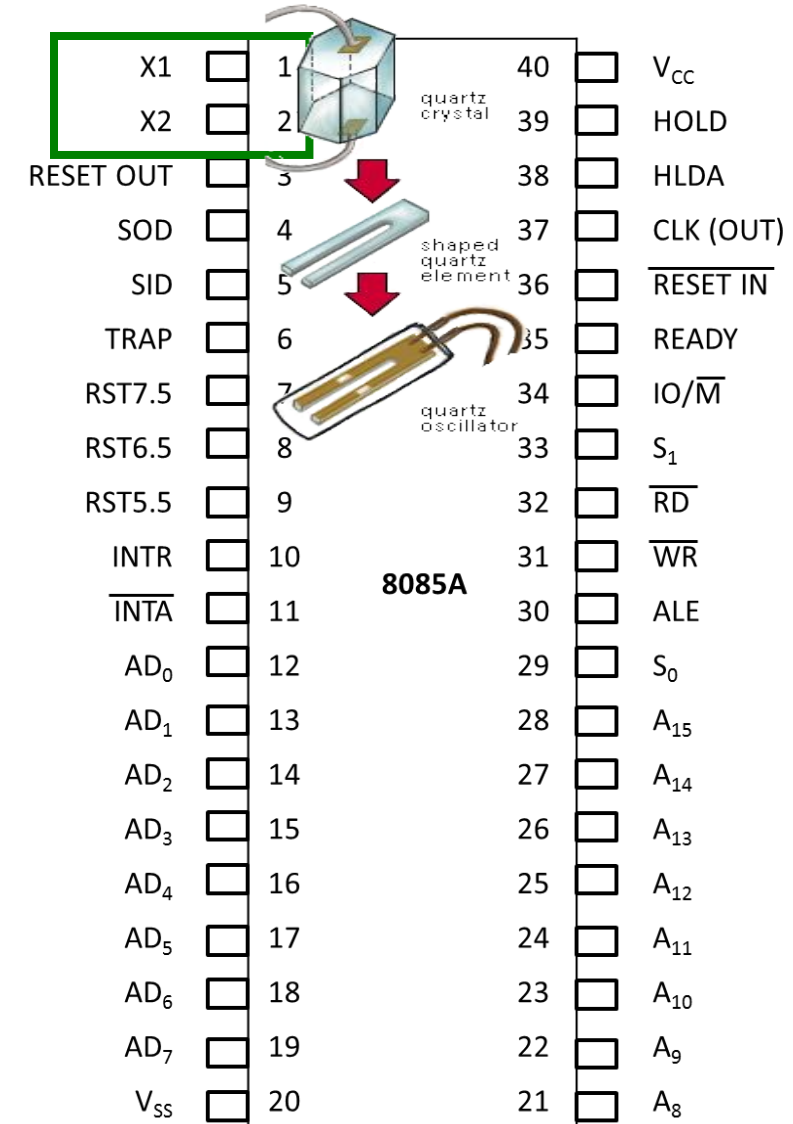
- **X1, X2** → Pin 1 & 2, Crystal Oscillator is connected at these two pins.
- The frequency is internally divided by two; therefore, to operate a system at **3MHz**, the crystal should have a frequency of **6MHz**.



8085 Pin Diagram: Power Supply & Frequency Signal

□ CLK (OUT) → Clock output

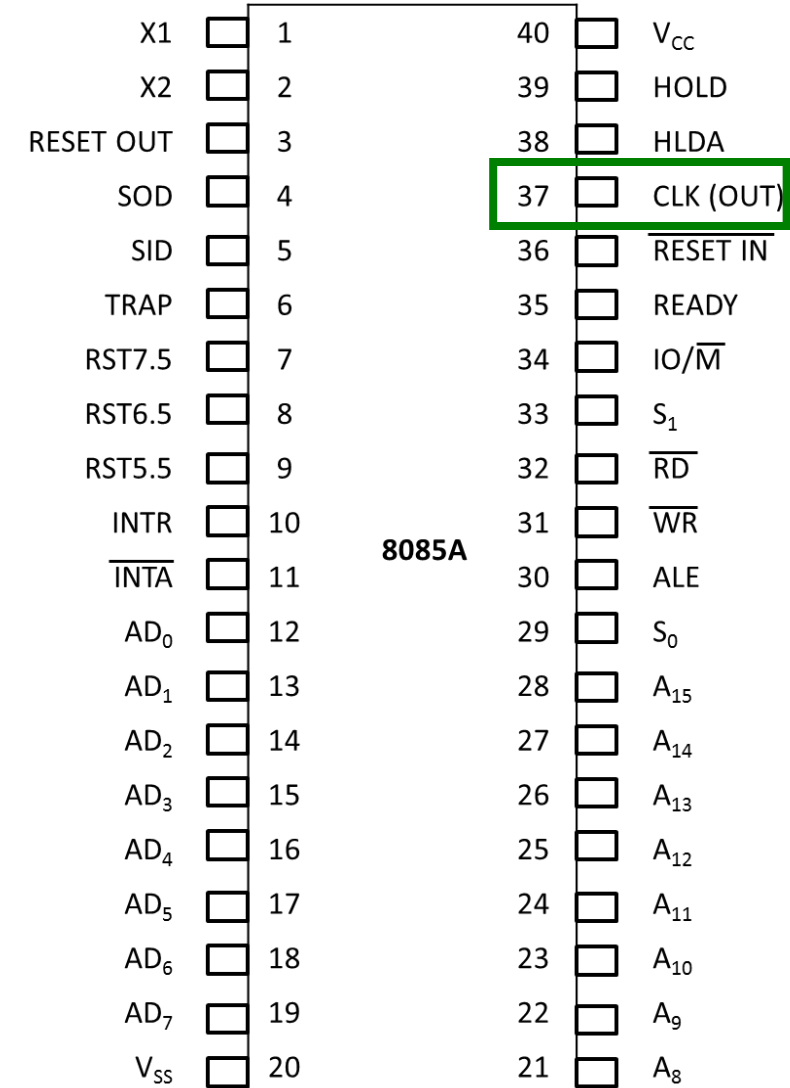 □ Pin 37: This signal is used as **system clock** for other I/O devices for **synchronization** with Microprocessor.




8085 Pin Diagram: Externally Initiated Signals

□ **INTR**(Input) → Interrupt Request


It is used for general purpose interrupt.

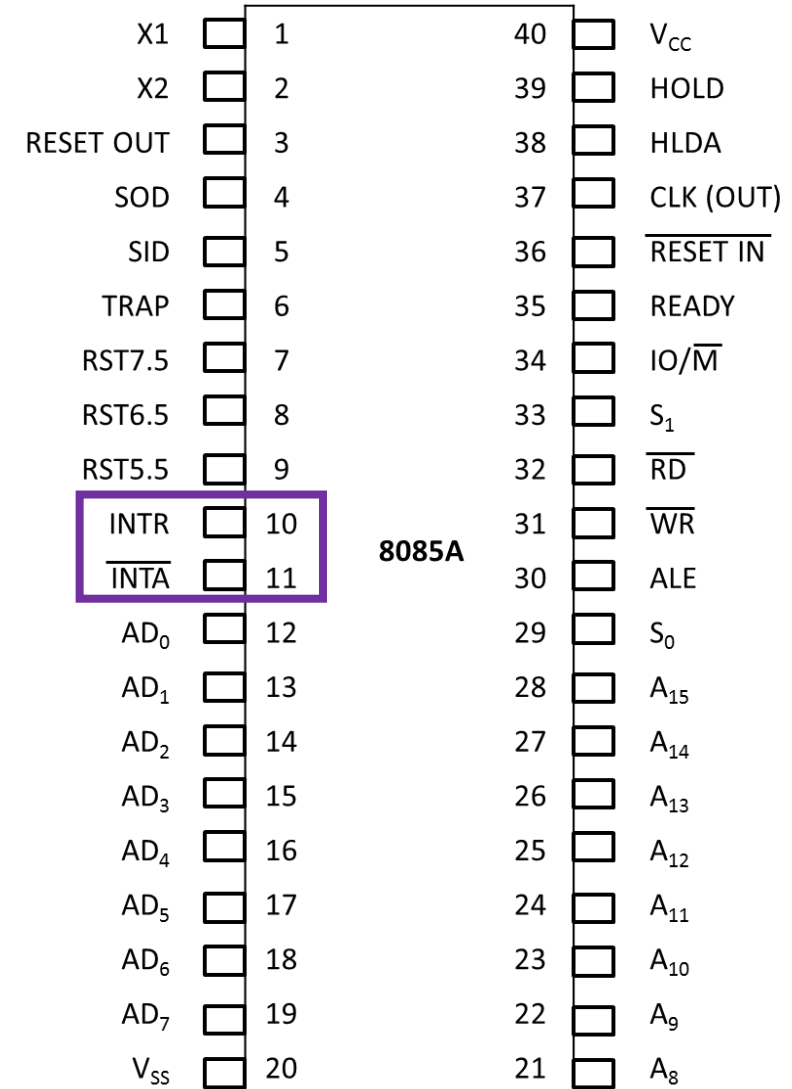□ **$\overline{\text{INTA}}$** (Output) → Interrupt Acknowledge.




8085 Pin Diagram: Externally Initiated Signals

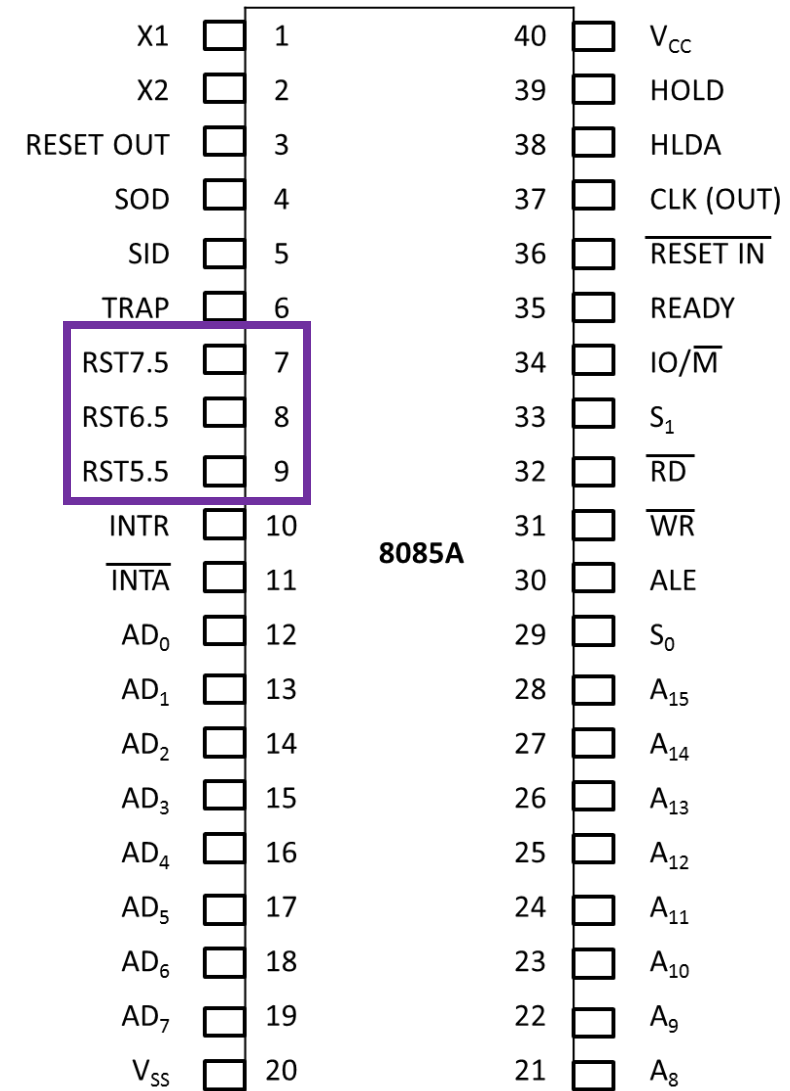- **RST7.5, RST6.5, RST5.5** (Input) → Restart Interrupts.
- These are **vector interrupts** that transfer the program control to specific **memory locations**.
- **RST7.5, RST6.5, RST5.5** have higher priorities than **INTR** interrupt.
- Among these 3 interrupts, the priority order (higher to lower) is **RST7.5, RST6.5, RST5.5** respectively.




8085 Pin Diagram: Externally Initiated Signals

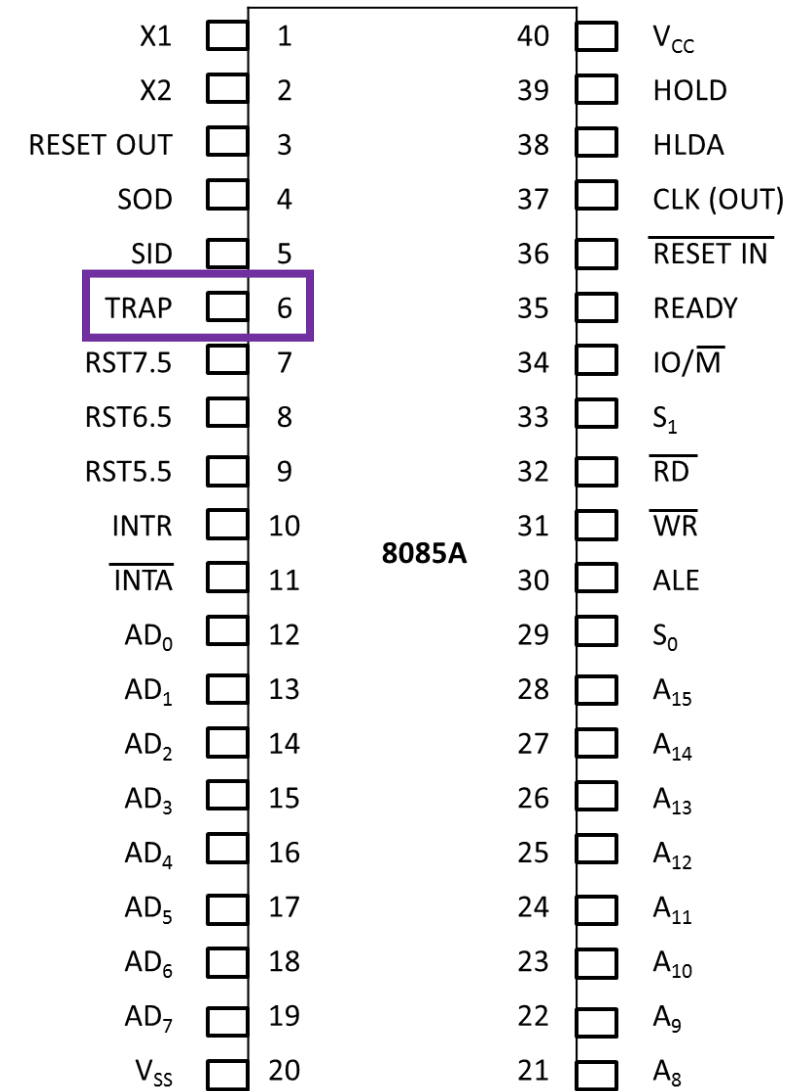□ **TRAP(Input)** → This is a **non maskable** interrupt & has the **highest priority**.



8085 Pin Diagram: Externally Initiated Signals

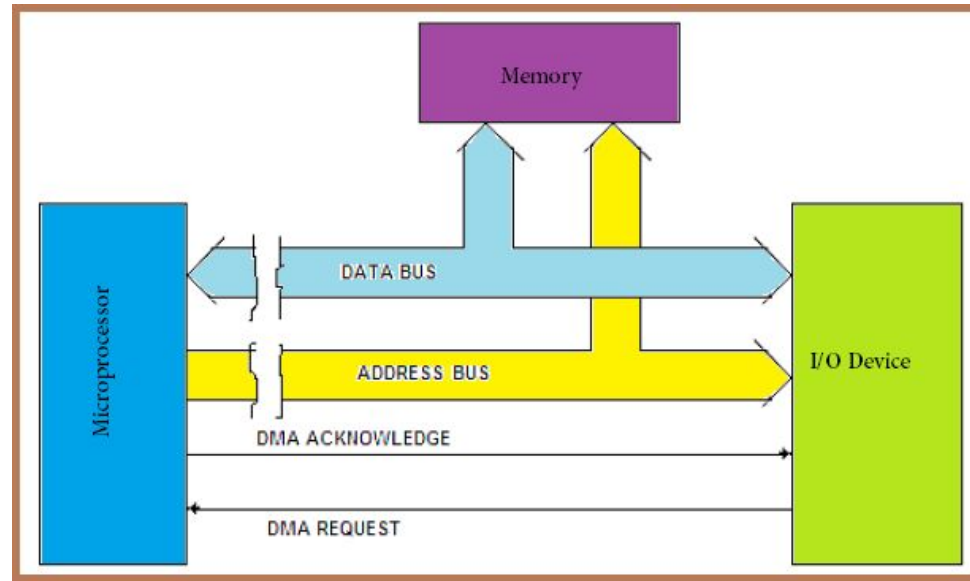- HOLD(Input)** → This signal indicates that a peripheral such as **DMA** Controller is requesting the use of address & data buses.
- HLDA(Output)** → Hold Acknowledge. This signal acknowledges the HOLD request.




X1	1	40	V _{CC}
X2	2	39	HOLD
RESET OUT	3	38	HLDA
SOD	4	37	CLK (OUT)
SID	5	36	RESET IN
TRAP	6	35	READY
RST7.5	7	34	IO/ \overline{M}
RST6.5	8	33	S ₁
RST5.5	9	32	\overline{RD}
INTR	10	31	\overline{WR}
\overline{INTA}	11	30	ALE
AD ₀	12	29	S ₀
AD ₁	13	28	A ₁₅
AD ₂	14	27	A ₁₄
AD ₃	15	26	A ₁₃
AD ₄	16	25	A ₁₂
AD ₅	17	24	A ₁₁
AD ₆	18	23	A ₁₀
AD ₇	19	22	A ₉
V _{SS}	20	21	A ₈

8085A


8085 Pin Diagram: Externally Initiated Signals

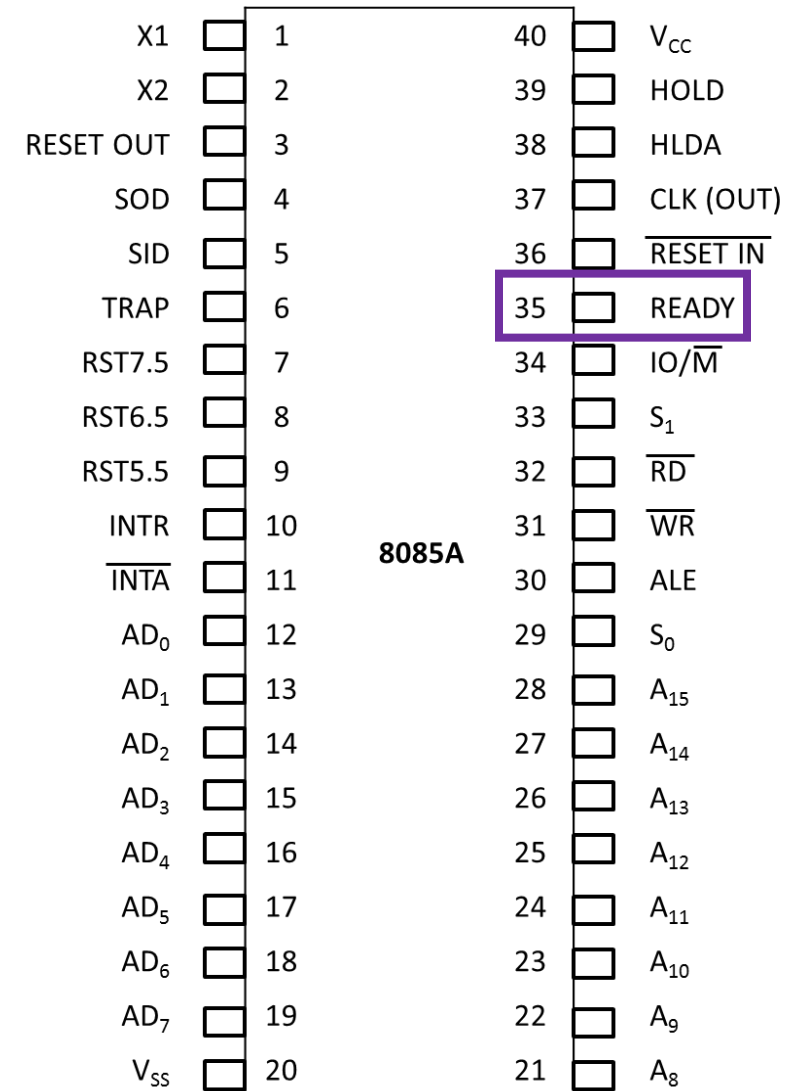- **READY**(Input) → This signal is used to **delay** the microprocessor read or write cycles until low-responding peripheral is ready to send or accept data.
- When the signal goes low, the microprocessor waits for an integral no. of clock cycles until **READY** signal goes high.



8085 Pin Diagram: Externally Initiated Signals

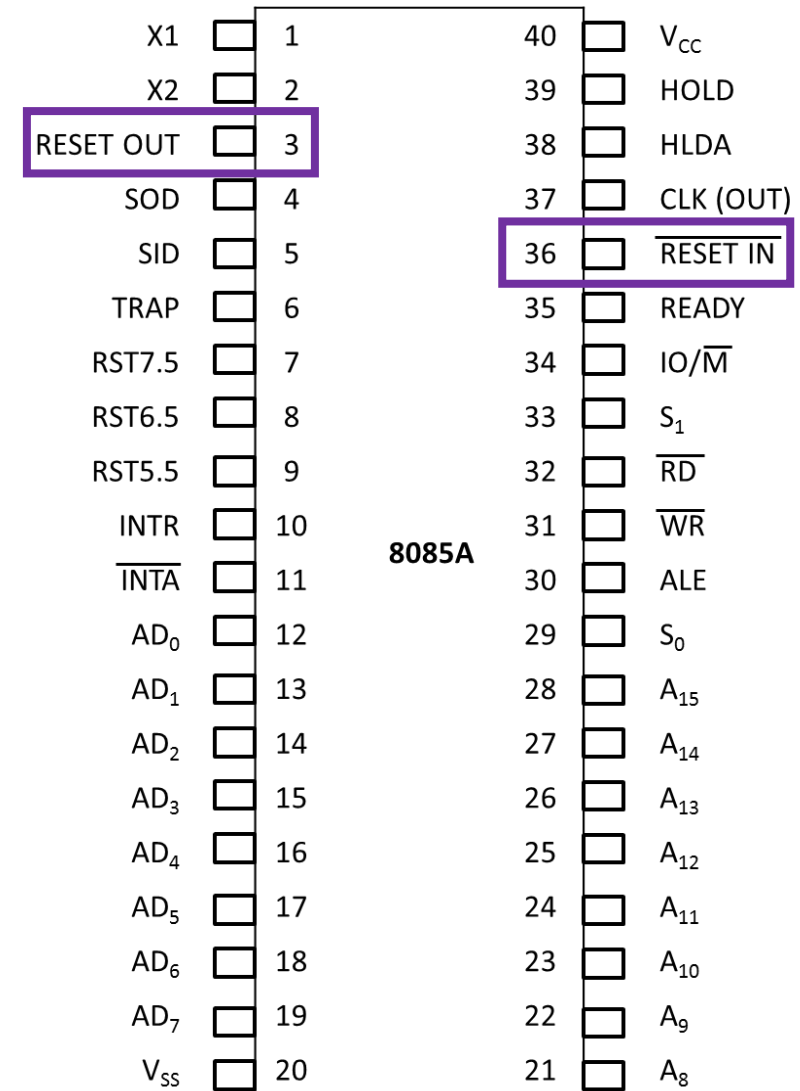- ❑ **RESET IN** (Input) → When the signal on this pin goes low, the Program Counter is set to zero, the buses are tri-stated & microprocessor is reset.
- ❑ **RESET OUT** (Output) → This signal indicates that microprocessor is being reset. The signal is also used to reset other devices.




8085 Pin Diagram: Serial I/O Ports

Two pins for serial transmission

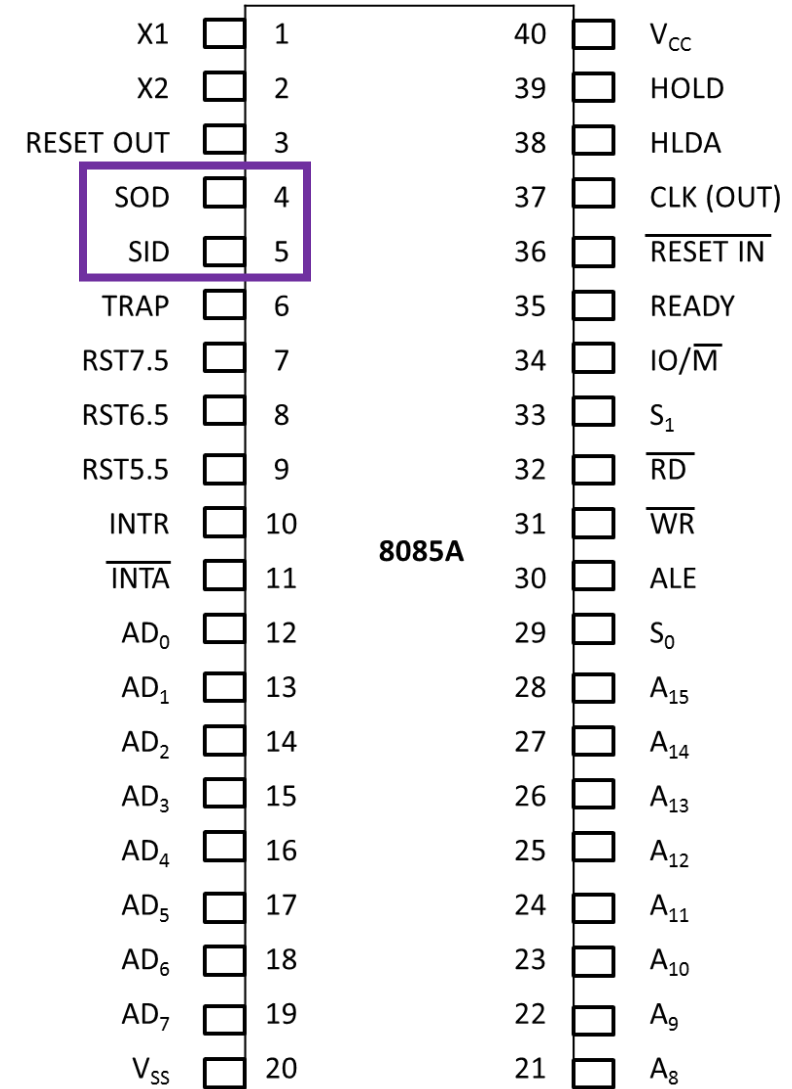1. **SID** (Serial Input Data)
2. **SOD** (Serial Output Data)

□ In serial transmission, data bits are sent over a single line, one bit at a time.





Sr.	GTU Questions	Marks	Year
1.	Draw and Explain the pin diagram of 8085 microprocessor.	7	Win-2019
2.	What is the use of ALE pin in 8085?	1	Sum-2019
3.	Explain the following pins of the 8085 microprocessor: IO/M , INTR, RESETIN	3	Win-2017

<input type="checkbox"/>	1	40	<input type="checkbox"/>
<input type="checkbox"/>	2	39	<input type="checkbox"/>
<input type="checkbox"/>	3	38	<input type="checkbox"/>
<input type="checkbox"/>	4	37	<input type="checkbox"/>
<input type="checkbox"/>	5	36	<input type="checkbox"/>
<input type="checkbox"/>	6	35	<input type="checkbox"/>
<input type="checkbox"/>	7	34	<input type="checkbox"/>
<input type="checkbox"/>	8	33	<input type="checkbox"/>
<input type="checkbox"/>	9	32	<input type="checkbox"/>
<input type="checkbox"/>	10	31	<input type="checkbox"/>
<input type="checkbox"/>	11	30	<input type="checkbox"/>
<input type="checkbox"/>	12	29	<input type="checkbox"/>
<input type="checkbox"/>	13	28	<input type="checkbox"/>
<input type="checkbox"/>	14	27	<input type="checkbox"/>
<input type="checkbox"/>	15	26	<input type="checkbox"/>
<input type="checkbox"/>	16	25	<input type="checkbox"/>
<input type="checkbox"/>	17	24	<input type="checkbox"/>
<input type="checkbox"/>	18	23	<input type="checkbox"/>

8085A


8085 Microprocessor signals

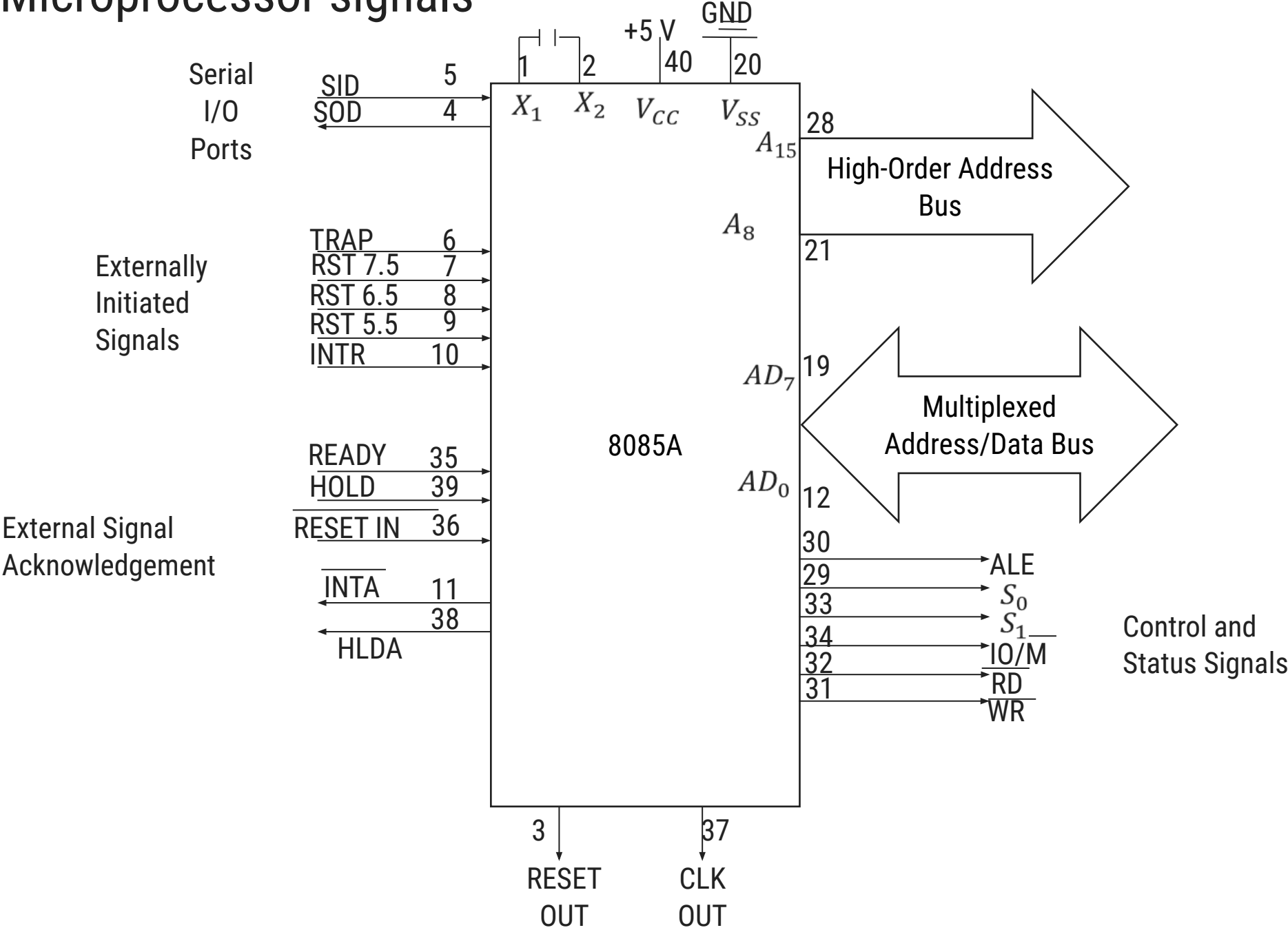

 


8085 Architecture/Block Diagram

8085 Block Diagram

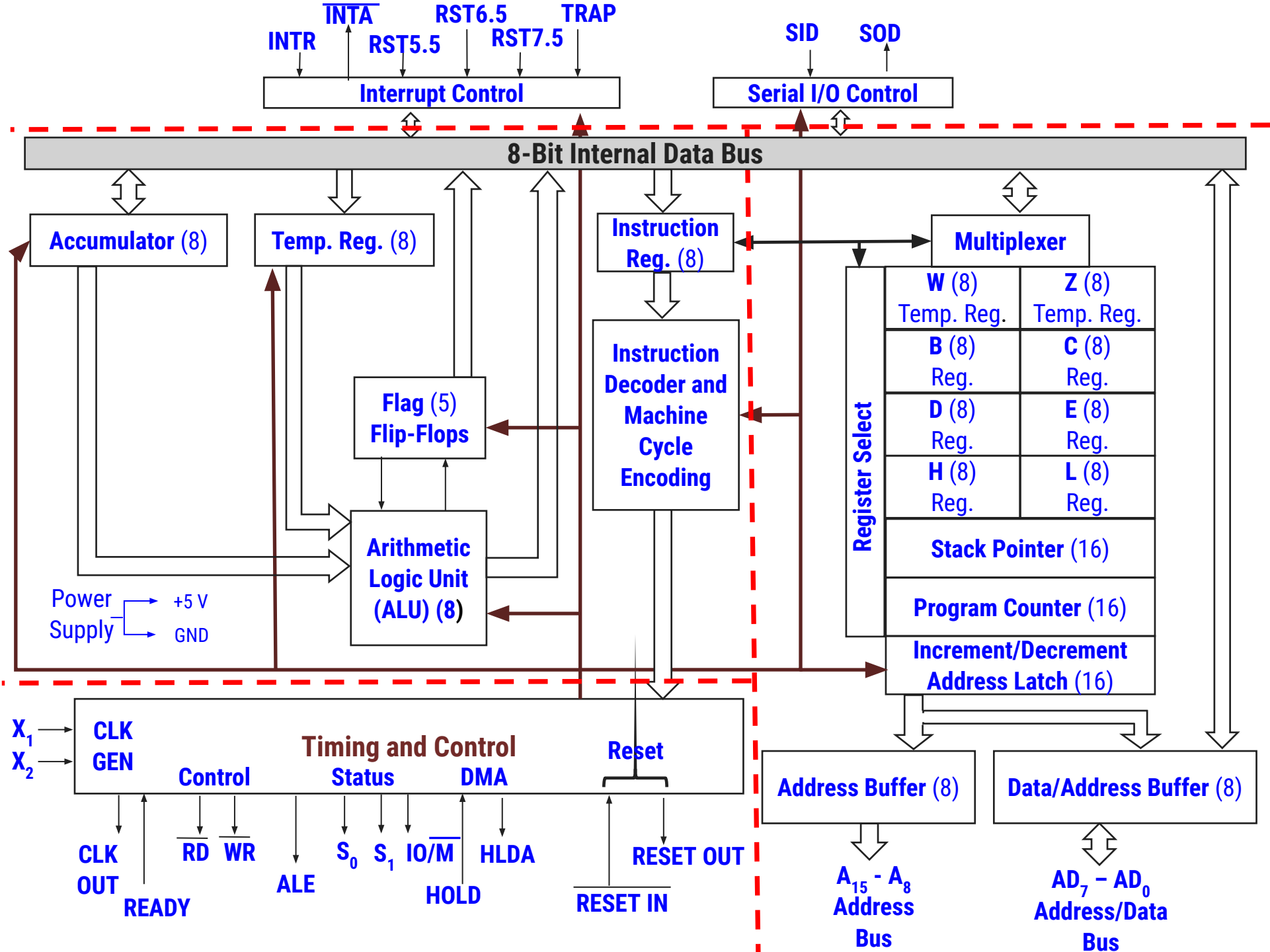

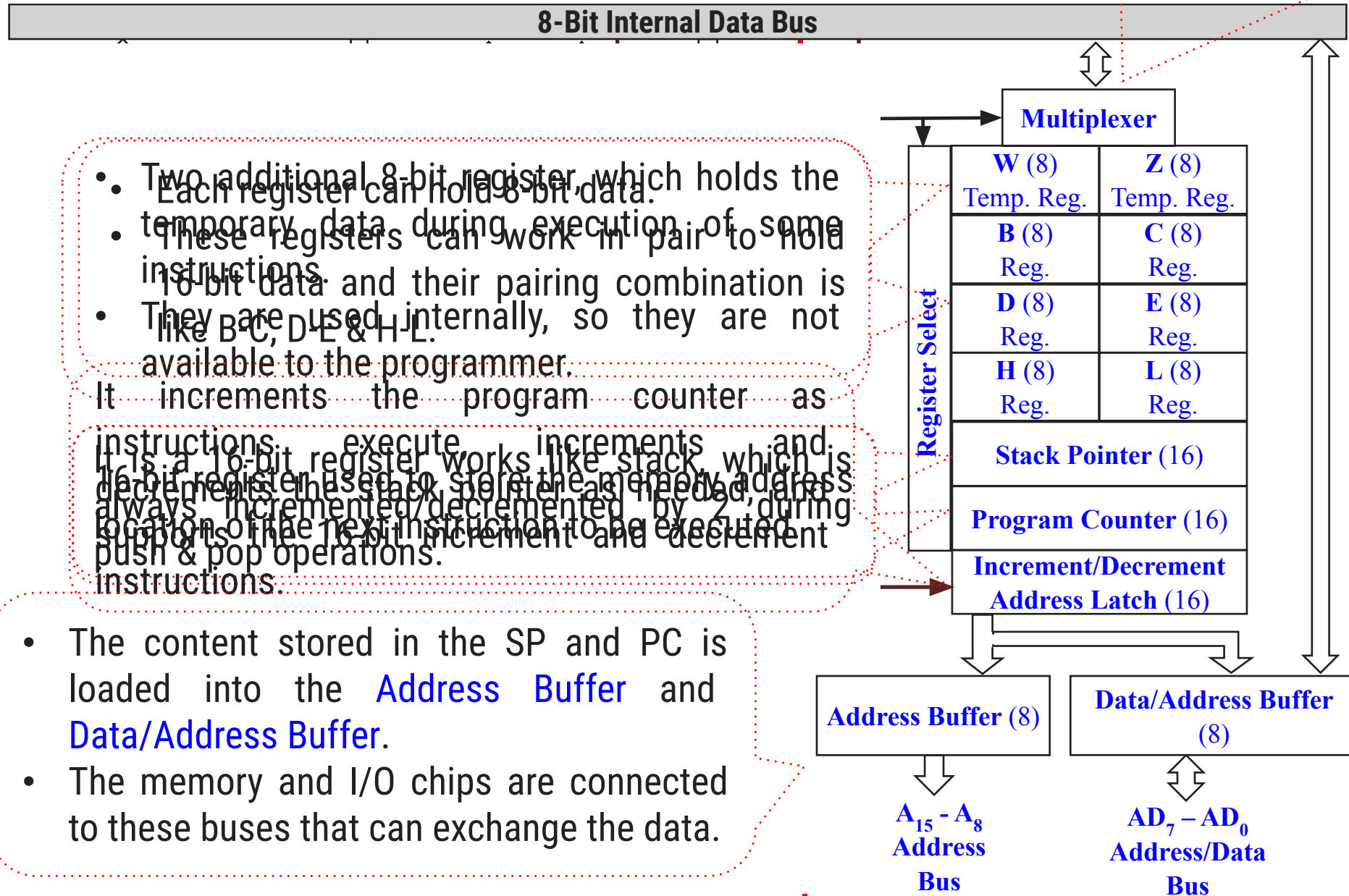A multiplexer pulls out the right group of bits, depending on the instruction.




8-Bit Internal Data Bus

This unit **synchronizes** all the microprocessor operations with the **clock** and generates **control signal** necessary for communication between


Read/write either to/from memory or peripherals
Perform any peripheral operation with microprocessor

 Frequency Control Signals with peripheral device
Shows read/write status to/from memory or I/O.




Signal to **RESET** microprocessor and other devices connected to it.

8-Bit Internal Data Bus

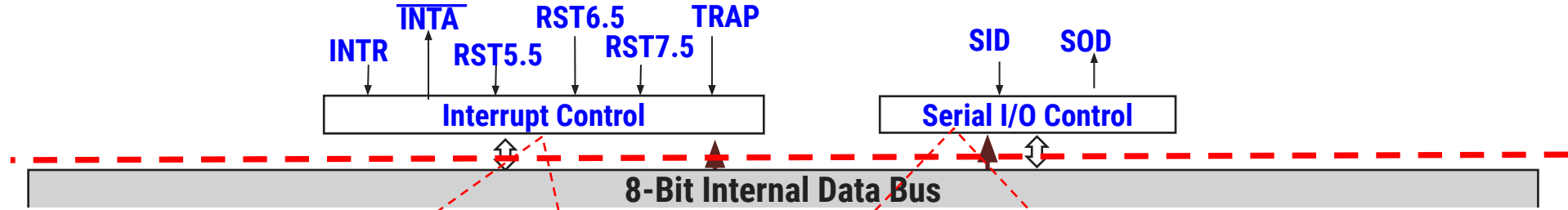


It controls the serial data communication by using two instructions:

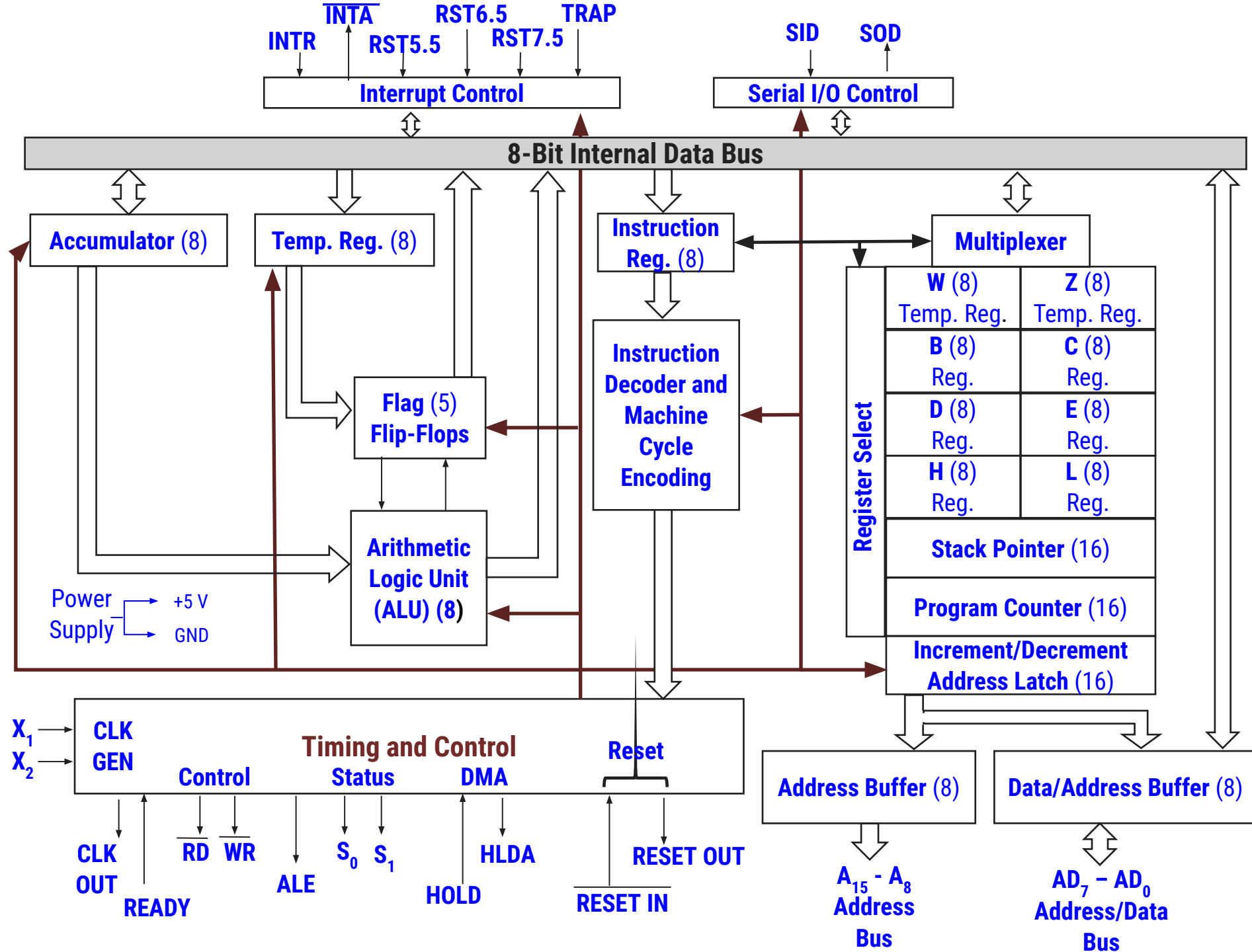- It controls the interrupts during a process.
- There are 5 interrupt signals in 8085 microprocessor. **TRAP, RST 7.5, RST 6.5, RST 5.5, INTR.**



GTU Exam Questions

Sr.	GTU Questions	Marks	Year
1.	Draw and explain the internal block diagram of 8085 microprocessor.	7	Sum-2019 Win-2018 Sum-2018

 

T-States, Machine and Instruction Cycle

T-States, Machine and Instruction Cycle

T-States

Operation performed in one **clock period**.

Machine Cycle


Time required by the microprocessor to complete an **operation**.

Instruction Cycle

Time required to complete **execution** of an instruction.


T-States

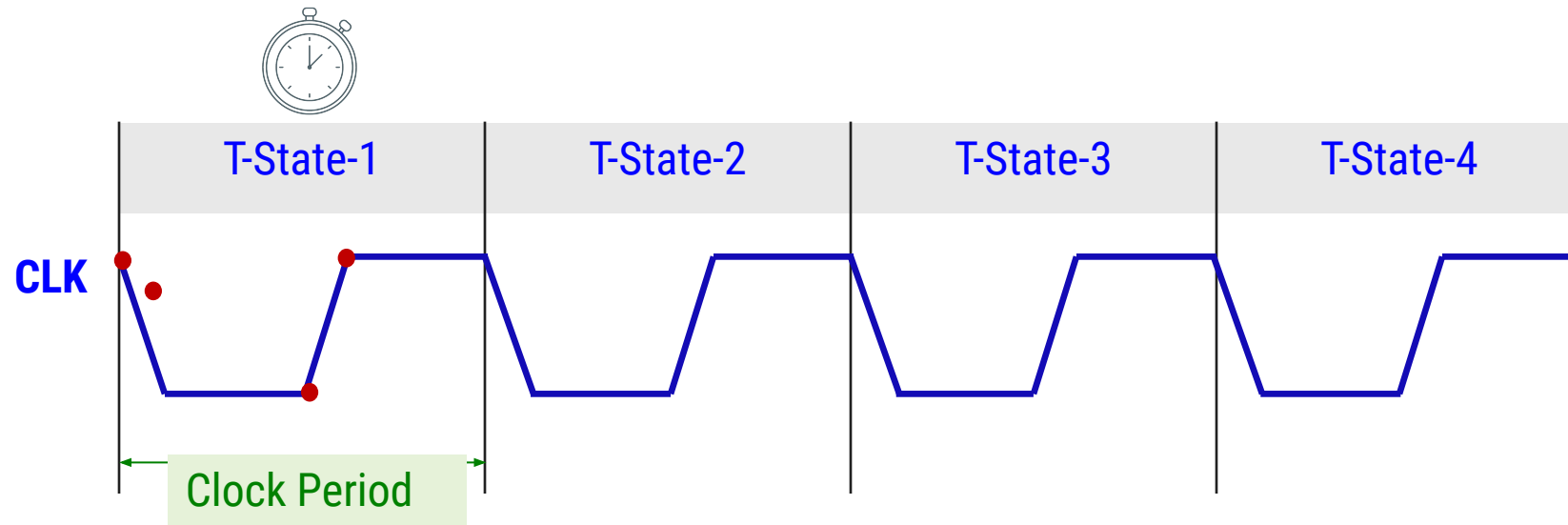- *"T-States are defined as operation performed in one clock period."*
- These **sub-divisions** are internal states synchronized with system clock & each T-state is **precisely** equal to **one clock period**.




Machine Cycle

 
- “Machine Cycle is defined as time required by the microprocessor to complete an operation.”
- This cycle may consist 3 to 6 T-states.
- The basic microprocessor operation such as **reading** a byte from **I/O port** or **writing** a byte to **memory**.



Instruction Cycle

 
- *"Instruction Cycle is defined as time required to complete execution of an instruction."*
- In 8085 microprocessor instruction cycle consists of 1 to 6 Machine Cycles or 1 to 6 operations.



 


T-States


Opcode Fetch

 


Machine Cycle

 


Instruction Cycle

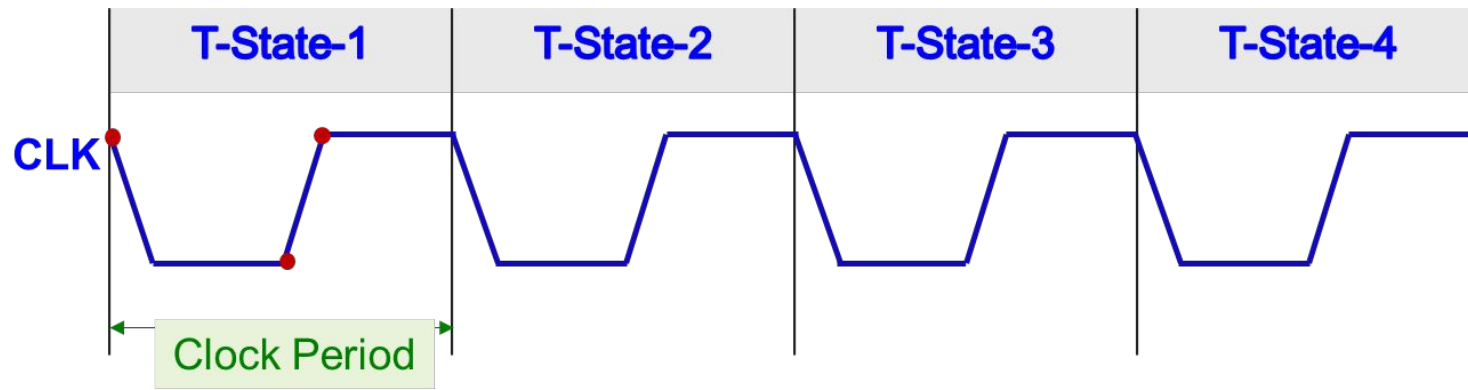


T-States

 

Machine Cycle

 


Instruction Cycle

 

Demultiplexing Address and Data Bus AD_0-AD_7

Demultiplexing AD₀-AD₇

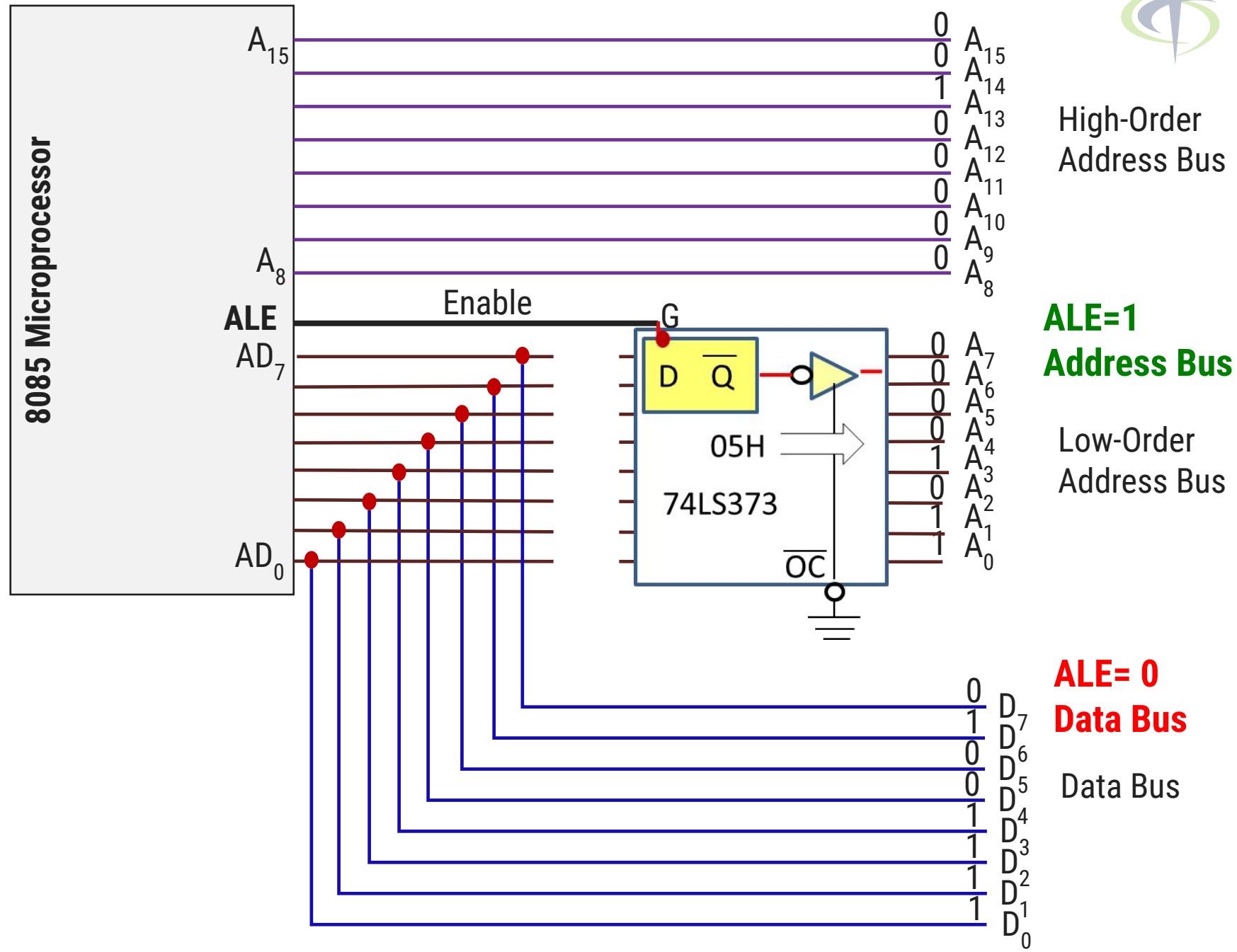


Demultiplexing AD_0 - AD_7

- The dual-purpose of the AD_0 - AD_7 pins is achieved through multiplexing.
- In simple words, multiplexing allows us to use the pins of a microprocessor for more than one function.
- **Advantage:** Since each pin can serve multiple purposes, the total number of pins can be reduced.

IC 74LS373

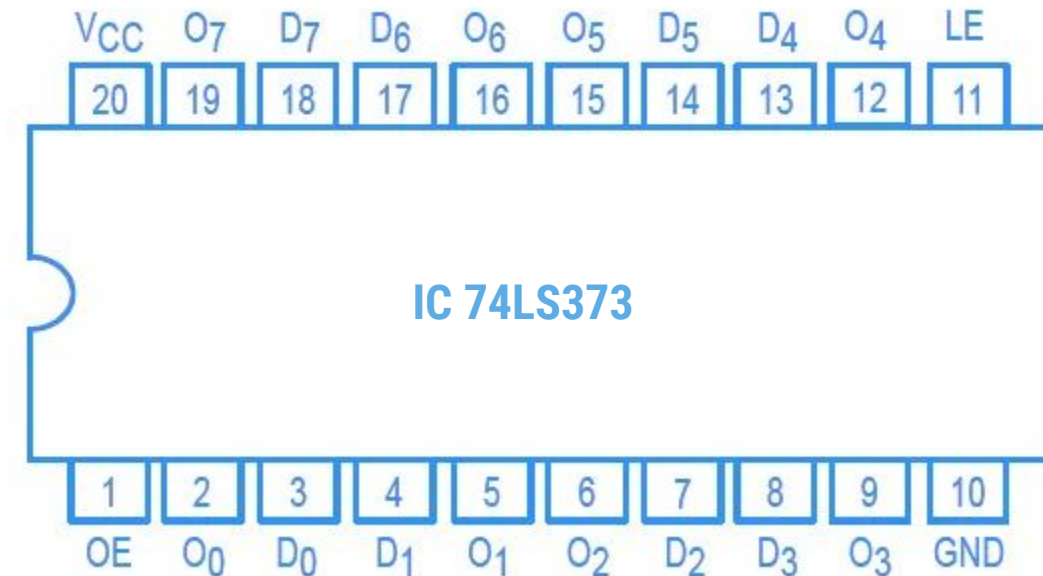- IC 74LS373 is an IC with 20 pins.
- it is a memory unit to hold one bit of data.




GTU Questions

Sr.	GTU Questions	Marks	Year
1.	How will the multiplexed address/data bus (AD_0 - AD_7) of the 8085 microprocessor be demultiplexed?	4	Win-2017




Timing Diagram


Timing Diagram

 


Timing Diagram: Opcode Fetch

 

Timing Diagram: Memory Read Cycle

 

Timing Diagram: Memory Write Cycle

 




Memory Interfacing

Memory structure

Block diagram of Memory Device: RAM

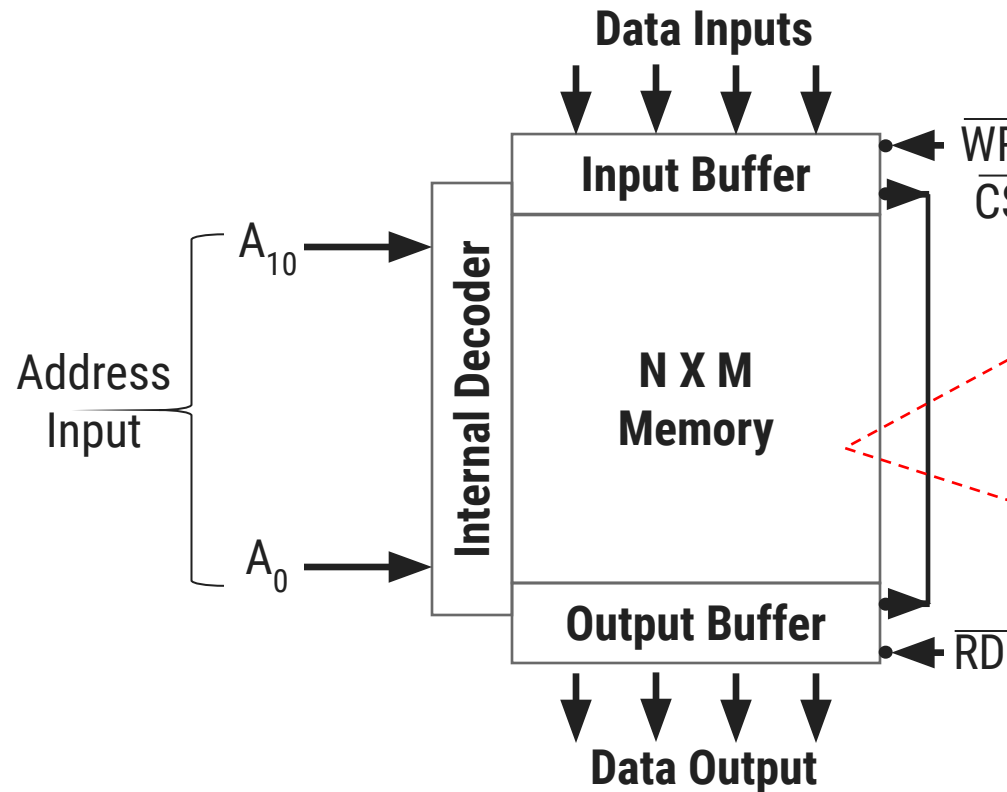

N=Number of Register

M=Word Length

E.g.

If a memory is having

address lines=13

data lines=8

then

1. Number of memory locations =

$$N=2^{13} = \mathbf{8192}$$

2. Word length M= **8 bit**

Therefore, N X M= 8192 X 8

Memory structure

No. of Lines	Memory size(bytes)	No. of Lines	Memory size(bytes)
1	2	9	512
2	4	10	1024=1k
3	8	11	2048=2k
4	16	12	4096=4k
5	32	13	8192=8k
6	64	14	16384=16k
7	128	15	32768=32k
8	256	16	65536=64k

2,048

HEX 800
 DEC 2,048
 OCT 4 000
 BIN 1000 0000 0000

65,535

HEX FFFF
 DEC 65,535
 OCT 177 777
 BIN 1111 1111 1111 1111

Memory Interfacing

- 8085 can access 64K of memory, thus address bus is of 16-bit.
- It is not always necessary to use full 64K address space. The total memory size depends upon the application.
- Generally EPROM is used as a program memory and RAM is used as data memory.
- When both are used then total 64K address will be shared by both.
- The capacity of program memory and data memory depends on the application.

Memory Interfacing

- It is not always necessary to select 1 EPROM and 1 RAM. We can have **multiple** EPROMs and multiple RAMs as per the requirement of application.
- We can place EPROM / RAM anywhere in full 64 Kbytes address space.
- Program memory (**EPROM**) should be located from address **0000H**, since reset address of 8085 microprocessor is **0000H**.
- It is not always necessary to locate **EPROM** and **RAM** in **consecutive** memory addresses.

Memory Interfacing: Example 1

Interface 4kB of EPROM with starting address from 0000H and 2kB of RAM with starting address followed by EPROM

Step-1: To calculate no. of EPROM and RAM chip required

Total EPROM required = 4kB

Chip size available = 4kB

No. of chips required = $4\text{kB}/4\text{kB}=1$

Total RAM required = 2kB

Chip Size Available = 2kB

No. of Chips required = $2\text{kB}/2\text{kB}=1$

Memory Interfacing: Example 1

Step-2: To calculate starting and ending address of EPROM

EPROM Chip-1:

Starting Address = **0000H**

Chip Size = 4kB (i.e. address Line=12, $m/m = 2^{12} = 4096B = 4k$)

Ending Address = **0FFFH**

Step-3: To calculate starting and ending address of RAM

RAM Chip-1:

Starting address = Ending address of EPROM +1
= 0FFFH+1
= **1000H**

Chip Size = 2kB = 07FFH

Ending address = 1000H+07FFH
= **17FFH**

4,095

HEX	FFF
DEC	4,095
OCT	7 777
BIN	1111 1111 1111

No. of Lines	Memory size(bytes)
9	512
10	1024=1k
11	2048=2k
12	4096=4k
13	8192=8k
14	16384=16k
15	32768=32k
16	65536=64k

Memory Interfacing: Example 1

Step-4: Memory Map		A 15	A 14	A 13	A 12	A 11	A 10	A 9	A 8	A 7	A 6	A 5	A 4	A 3	A 2	A 1	A 0
EPROM 4k	Start Address 0000 H	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 0FFF H	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1
RAM 2k	Start Address 1000 H	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 17FF H	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1

EPROM chip size = 4kB & RAM chip size = 2kB

∴ smaller chip size RAM = 2kB = 2^{11}

Thus neglect lower 11 address lines (A_0 to A_{10}), and consider A_{11} to A_{15} for Decoding.

Memory Interfacing: Example 1

		A	A	A	A	A	A	A	A	A	A	A	A	A	A	A	
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
EPROM	Start Address 0000 H	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 0FFF H	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1

EPROM

- Required Address Lines: A_{11} to A_{15} .
- Now, EPROM has two Possibilities, either 00000 b or 00001 b.
- Therefore, it requires Y_0 and Y_1 outputs of decoder.


Memory Interfacing: Example 1

		A	A	A	A	A	A	A	A	A	A	A	A	A	A	A	A
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
EPROM	Start Address 0000 H	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 0FFF H	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1
RAM	Start Address 1000 H	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 17FF H	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1

RAM has **00010** b, hence it requires Y_2 output of decoder.

Memory Interfacing: Example 1 Implementation

Step-5:

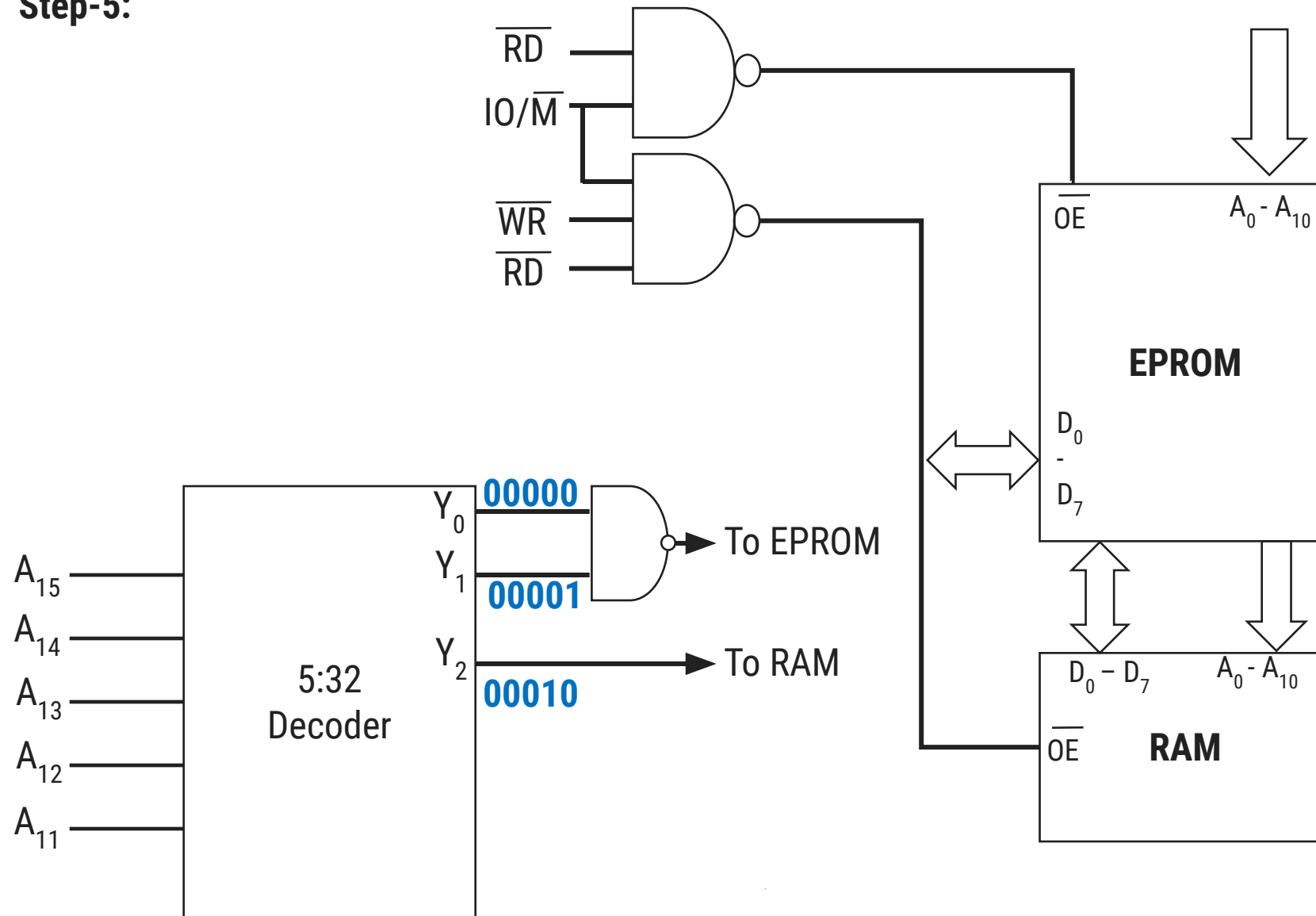

Memory Interfacing: Example 2

Interface **16kB** of **EPROM** with **chip size** of **8kB** and starting address from **0000H** and **8kB** of **RAM** with starting address followed by **EPROM**.

Step-1: To calculate no. of EPROM and RAM chip required

Total **EPROM** required = 16kB

Chip size available = 8kB

No. of chips required = $16\text{kB}/8\text{kB} = 2$

Total **RAM** required = 8kB

Chip size available = 8kB

No. of chips required = $8\text{kB}/8\text{kB} = 1$

Memory Interfacing: Example 2

Step-2: To calculate starting and ending address of EPROM

EPROM Chip-1:

Starting Address = **0000H**

Chip Size = 8kB (i.e. address Line=13, $m/m=2^{13} = 8192B = 8k$)

Ending Address = **1FFFH**

HEX 1FFF
DEC 8,191
OCT 17 777
BIN 0001 1111 1111 1111

8,191

EPROM Chip-2:

Starting Address = **1FFFH + 1 = 2000H**

Chip Size = 1FFFH

Ending Address = **2000+1FFFH = 3FFFH**

No. of Lines	Memory size(bytes)
9	512
10	1024=1k
11	2048=2k
12	4096=4k
13	8192=8k
14	16384=16k
15	32768=32k
16	65536=64k

Memory Interfacing: Example 2

Step-3:RAM Chip-1:

Starting Address = EPROM ending address + 1

Starting Address = 3FFFH+1 = **4000H**

Chip Size = 8kB (i.e. address Line =13, $m/m=2^{13} = 8192B = 8k$)

Chip Size = 1FFFH

Ending Address = 4000h+1FFFH = **5FFFH**

Memory Interfacing: Example 2


Step-4: Memory Map		A	A	A	A	A	A	A	A	A	A	A	A	A	A	A	A
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
EPROM1	Start Address 0000 H	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 1FFF H	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1
EPROM2	Start Address 2000 H	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 3FFF H	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
RAM	Start Address 4000 H	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 5FFF H	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1

Memory Interfacing: Example 2

Step-5: Interface Implementation

- EPROM chip size = RAM chip size = 8kB = 2^{13}
- Therefore, neglect lower 13 address lines (i.e. A_0 to A_{12}) and consider only A_{13} to A_{15} for decoding.

EPROM CHIP-01	000
EPROM CHIP-02	001
RAM CHIP-01	010

 


Memory Interfacing: Example 2

Step-4: Memory Map		A	A	A	A	A	A	A	A	A	A	A	A	A	A	A	A
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
EPROM1	Start Address 0000 H	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 1FFF H	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1
EPROM2	Start Address 2000 H	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 3FFF H	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
RAM	Start Address 4000 H	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 5FFF H	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1

Memory Interfacing: Example 2 Implementation

Step-5:

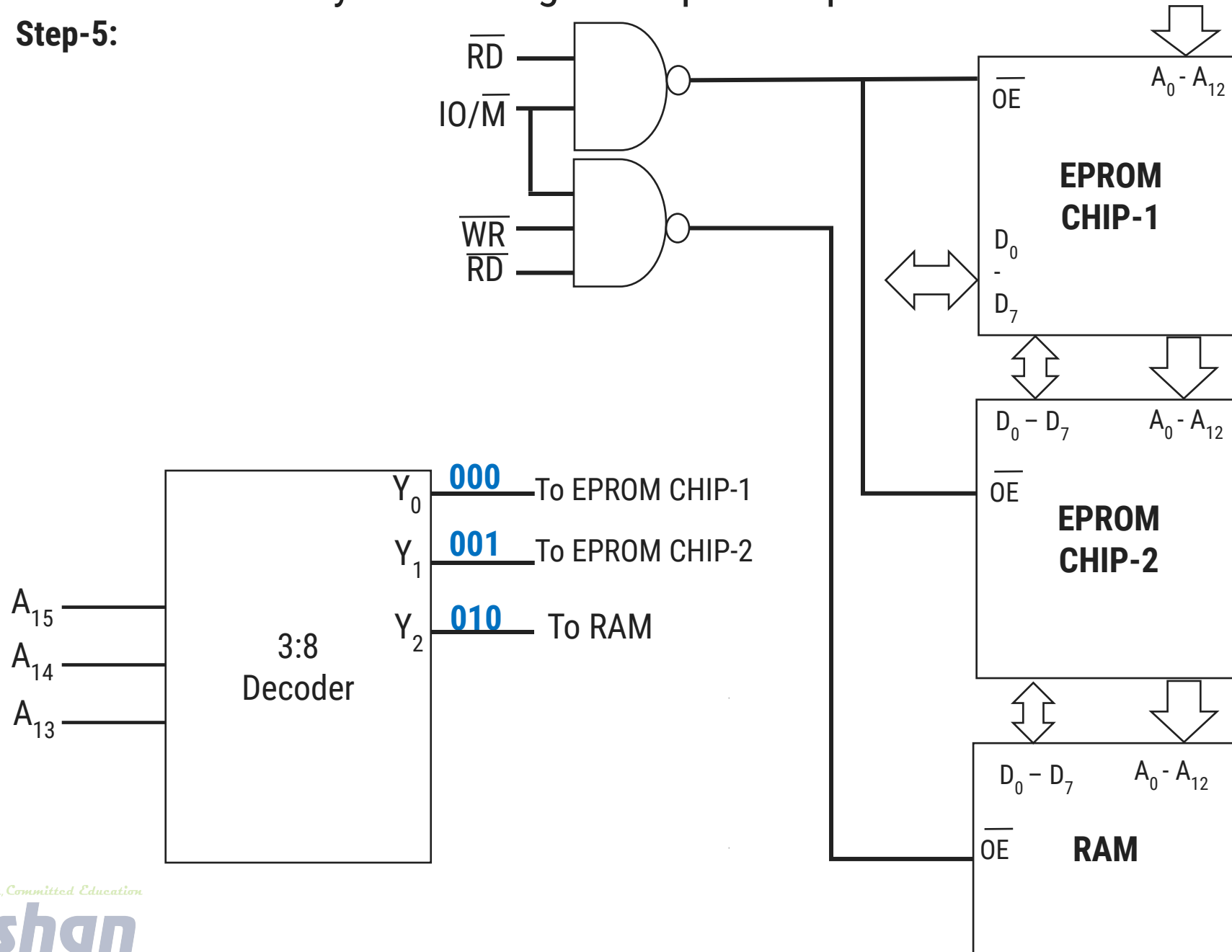

Exercise: Memory Interface Example


1. Draw the interfacing of a **4KB** EPROM having a starting address 2000h and **two 2KB** static RAMs having starting addresses 4000h and 8000h, respectively, with 8085 microprocessor.
2. Design an 8085 microprocessor system such that it should contain **16KB** of EPROM and **4KB** of RAM with starting addresses 0000H and 4000H respectively. Use two **8KB** of EPROMs (2764) and two **2KB** of RAMs (6116) for this system.

Exercise: Example 1

Step-4: Memory Map		A	A	A	A	A	A	A	A	A	A	A	A	A	A	A	A
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
EPROM1	Start Address 2000 H	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 2FFF H	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1
RAM 1	Start Address 4000 H	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 47FF H	0	1	0	0	0	1	1	1	1	1	1	1	1	1	1	1
RAM 2	Start Address 8000 H	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	End Address 87FF H	1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1

Exercise: Example 1

Step-5:

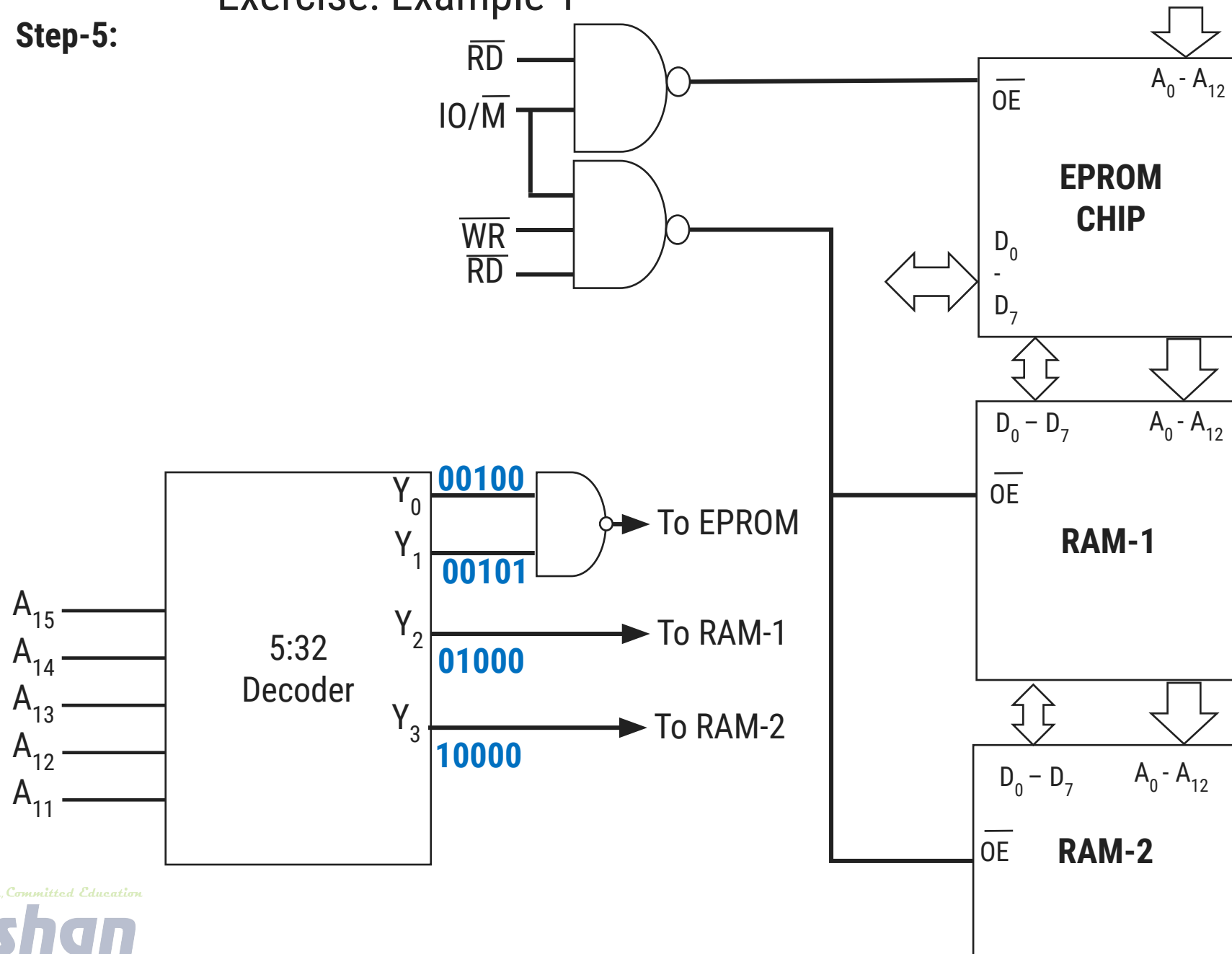


Exercise: Example 2

[illegible]

Exercise: Example 2

Step-5:

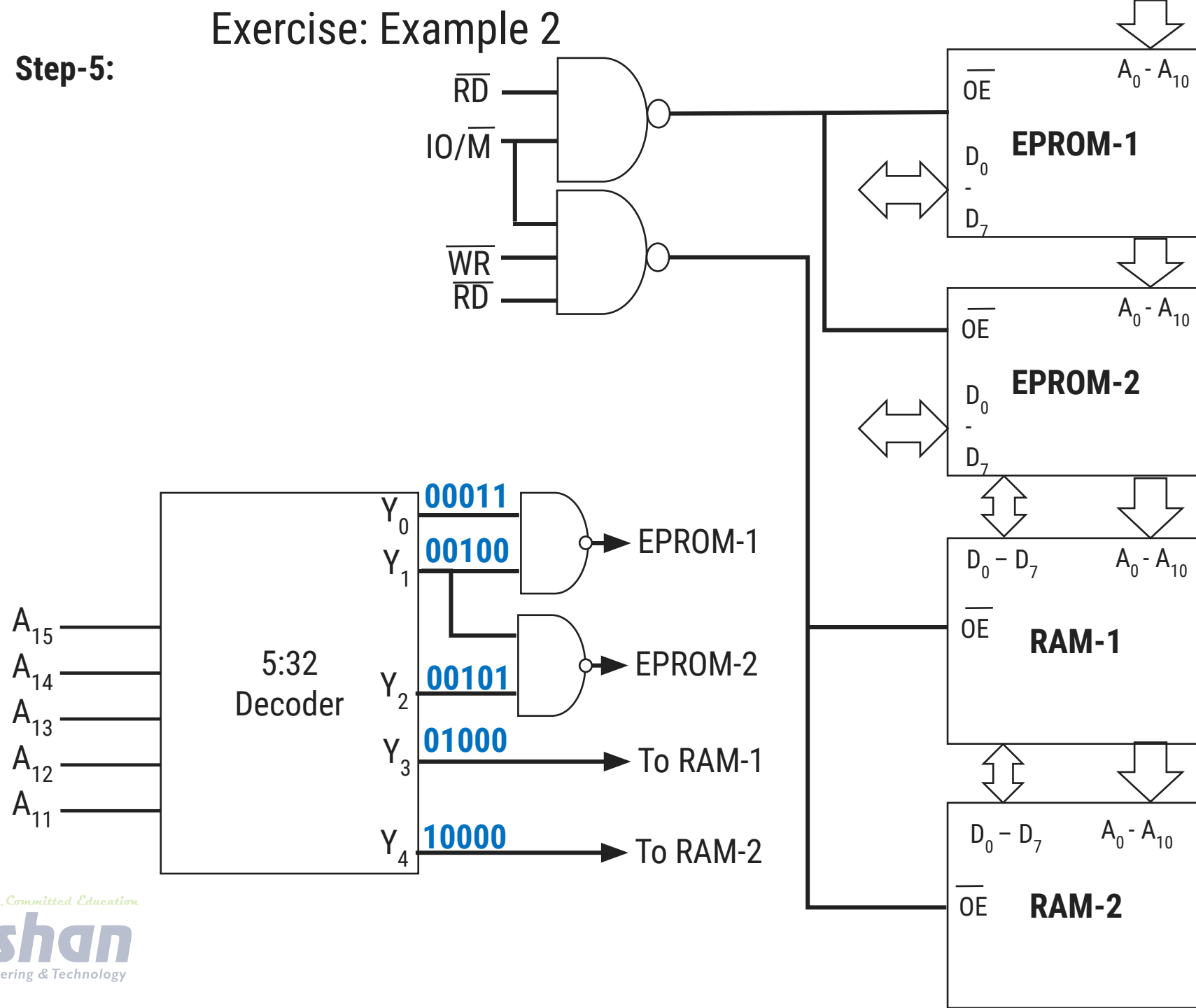




Generating Control Signals


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	0	Invalid
0	0	1	$\overline{\text{MEMR}}$

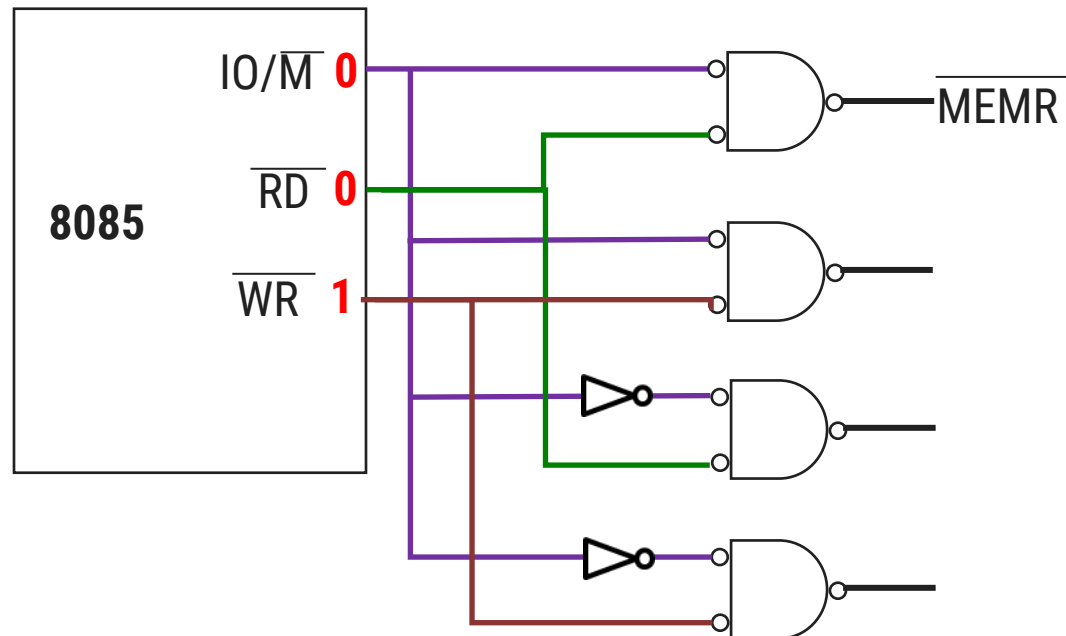


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	0	Invalid
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$

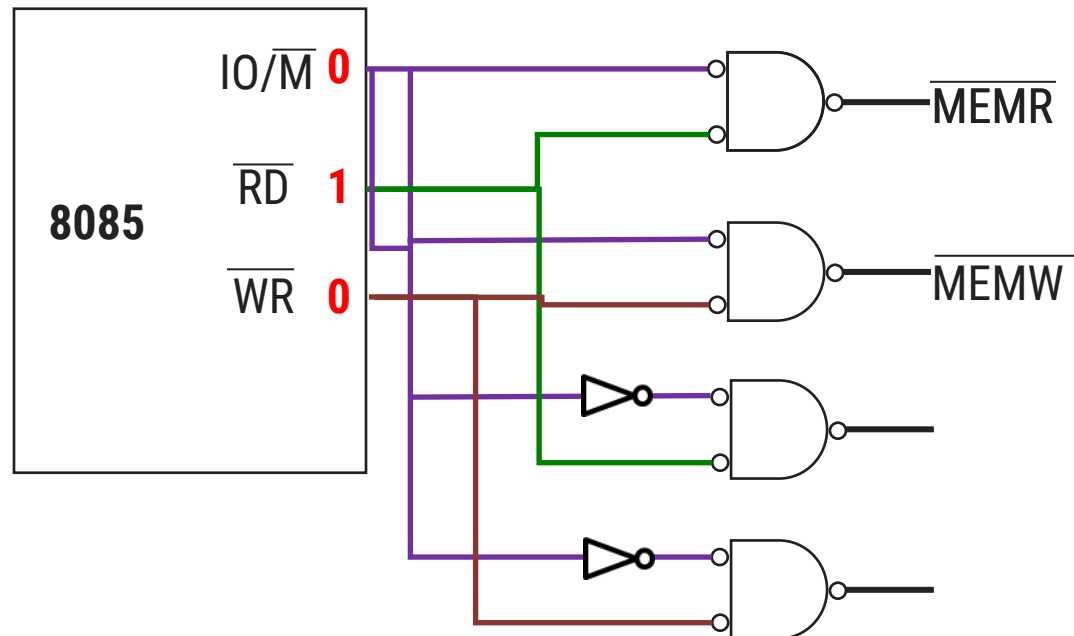


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	0	Invalid
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$
0	1	1	NOP

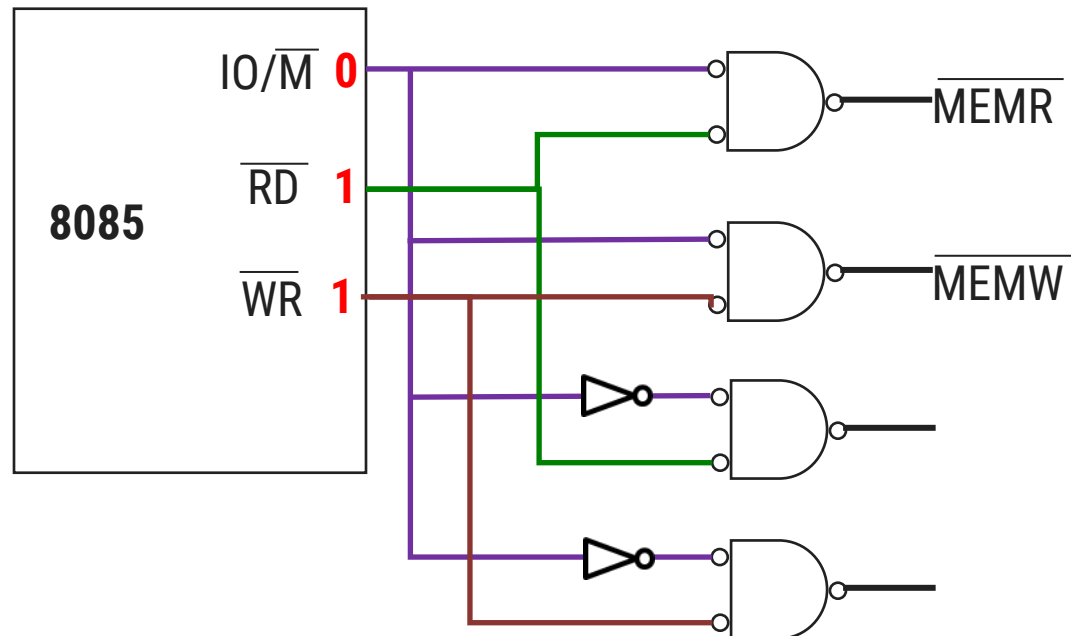


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$
0	1	1	NOP
1	0	0	Invalid

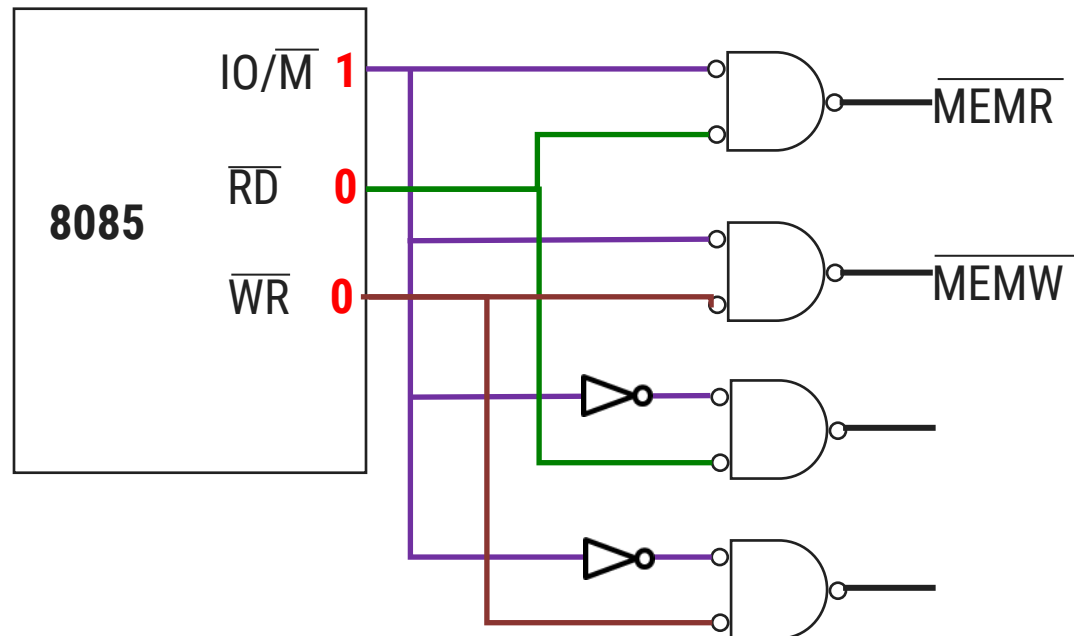


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$
0	1	1	NOP
1	0	1	$\overline{\text{IOR}}$

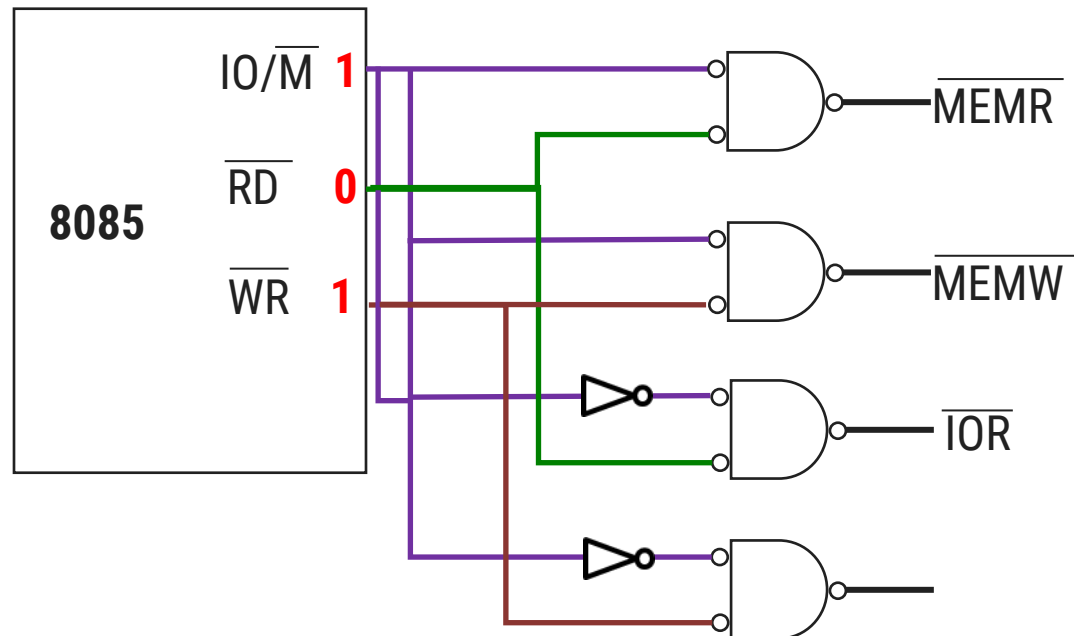


Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$
0	1	1	NOP
1	0	1	$\overline{\text{IOR}}$
1	1	0	$\overline{\text{IOW}}$

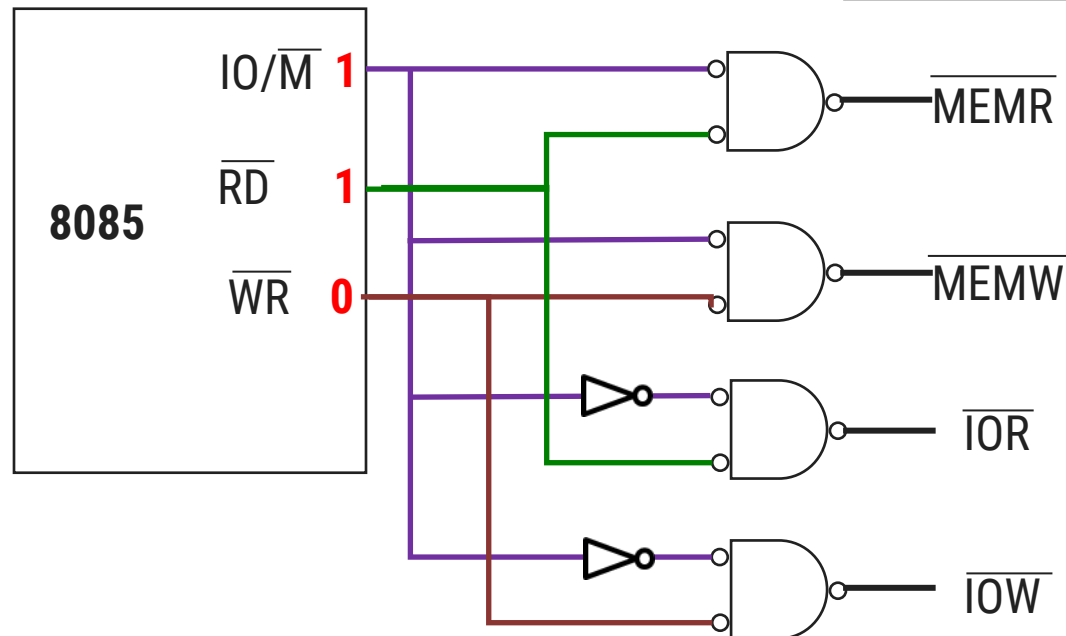

Generating Control Signals

$\text{IO}/\overline{\text{M}}$	$\overline{\text{RD}}$	$\overline{\text{WR}}$	Operation
0	0	1	$\overline{\text{MEMR}}$
0	1	0	$\overline{\text{MEMW}}$
0	1	1	NOP
1	0	1	$\overline{\text{IOR}}$
1	1	0	$\overline{\text{IOW}}$
1	1	1	NOP

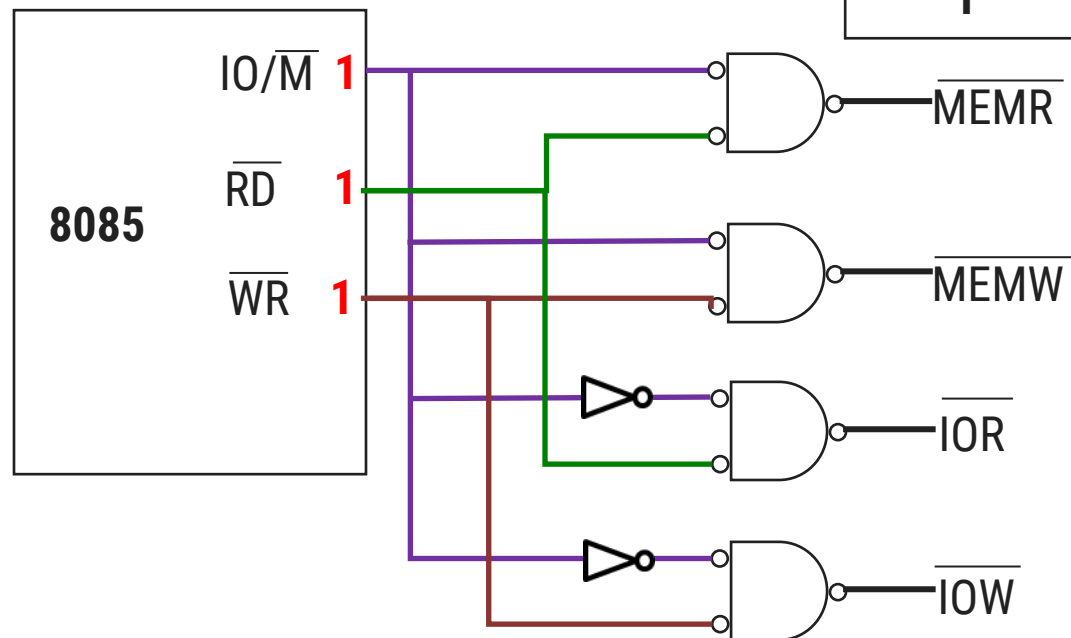

Generating Control Signals

$\overline{IO/M}$	\overline{RD}	\overline{WR}	Operation
0	0	0	HLT
0	0	1	\overline{MEMR}
0	1	0	\overline{MEMW}
0	1	1	NOP
1	0	0	HLT
1	0	1	\overline{IOR}
1	1	0	\overline{IOW}
1	1	1	NOP

GTU Exam Questions

Sr. GTU Questions

1. How will the multiplexed address/data bus (AD0-AD7) of the 8085 microprocessor be demultiplexed?
2. Explain the flag register of the 8085 microprocessor with examples.
3. Draw the interfacing of a 4KB EPROM having a starting address 2000h and two 2KB static RAMs having starting addresses 4000h and 8000h, respectively, with 8085 microprocessor. Use demultiplexed address/data lines and use 3-to-8 decoder (74LS138).
4. Draw and explain the internal block diagram of 8085 microprocessor.
5. List the sequence of events that occurs when the 8085 MPU reads from memory.
6. Explain 8085 Programming Model and Flag Register.
7. Discuss the programming model of 8085 μ P with the help of suitable diagram.
8. Draw and Explain the pin diagram of 8085 microprocessor.

References



Book: Microprocessor Architecture, Programming, and Applications with the 8085, Ramesh S.
Gaonkar Pub: Penram International



Thank You

